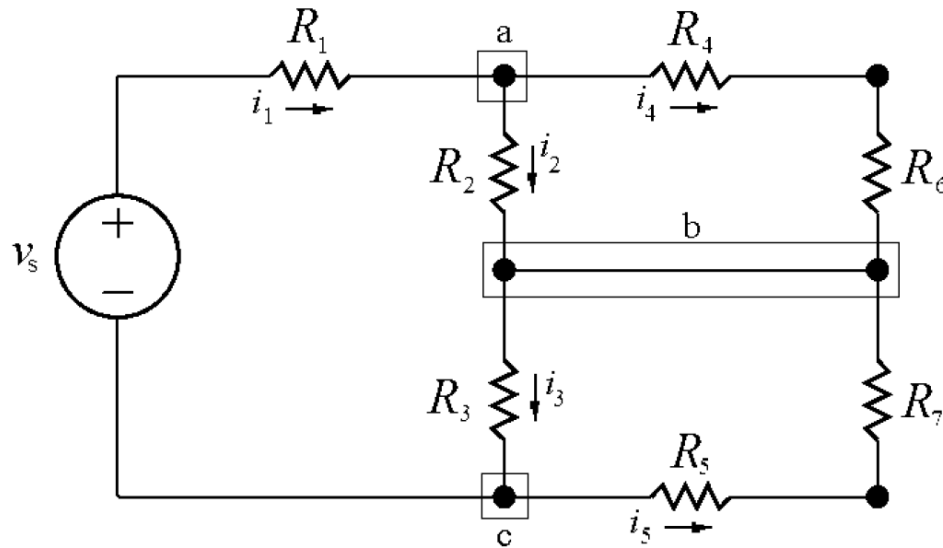


## Circuits 2

### Home Work # 0 Solution

- P 4.3 [a] There are eight circuit components, seven resistors and the voltage source. Therefore there are **eight** unknown currents. However, the voltage source and the  $R_1$  resistor are in series, so have the same current. The  $R_4$  and  $R_6$  resistors are also in series, so have the same current. The  $R_5$  and  $R_7$  resistors are in series, so have the same current. Therefore, we only need 5 equations to find the 5 distinct currents in this circuit.

[b]



There are three essential nodes in this circuit, identified by the boxes. At two of these nodes you can write KCL equations that will be independent of one another. A KCL equation at the third node would be dependent on the first two. Therefore there are **two** independent KCL equations.

- [c] Sum the currents at any two of the three essential nodes a, b, and c. Using nodes a and c we get

$$-i_1 + i_2 + i_4 = 0$$

$$i_1 - i_3 + i_5 = 0$$

- [d] There are three meshes in this circuit: one on the left with the components  $v_s$ ,  $R_1$ ,  $R_2$  and  $R_3$ ; one on the top right with components  $R_2$ ,  $R_4$ , and  $R_6$ ; and one on the bottom right with components  $R_3$ ,  $R_5$ , and  $R_7$ . We can write KVL equations for all three meshes, giving a total of **three** independent KVL equations.


$$\text{P 4.10 [a]} \quad \frac{v_o - v_1}{R} + \frac{v_o - v_2}{R} + \frac{v_o - v_3}{R} + \cdots + \frac{v_o - v_n}{R} = 0$$

$$\therefore nv_o = v_1 + v_2 + v_3 + \cdots + v_n$$

$$\therefore v_o = \frac{1}{n}[v_1 + v_2 + v_3 + \cdots + v_n] = \frac{1}{n} \sum_{k=1}^n v_k$$

$$\text{[b]} \quad v_o = \frac{1}{3}(100 + 80 - 60) = 40 \text{ V}$$

P 4.15 [a]

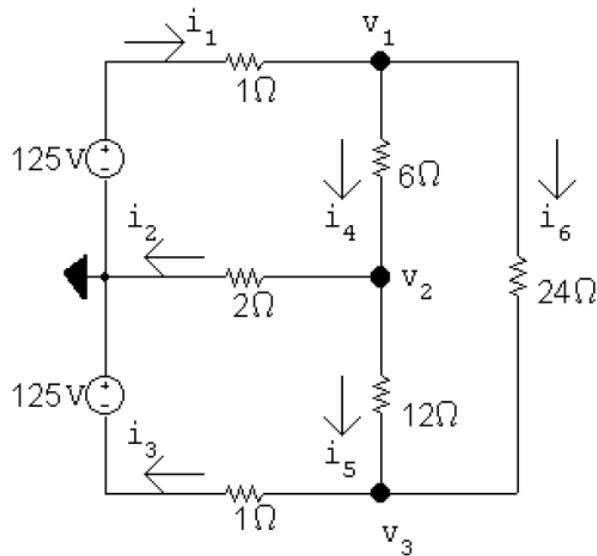

$$\frac{v_1 - 125}{1} + \frac{v_1 - v_2}{6} + \frac{v_1 - v_3}{24} = 0$$

$$\frac{v_2 - v_1}{6} + \frac{v_2}{2} + \frac{v_2 - v_3}{12} = 0$$

$$\frac{v_3 + 125}{1} + \frac{v_3 - v_2}{12} + \frac{v_3 - v_1}{24} = 0$$

In standard form:

$$\begin{aligned} v_1 \left( \frac{1}{1} + \frac{1}{6} + \frac{1}{24} \right) + v_2 \left( -\frac{1}{6} \right) + v_3 \left( -\frac{1}{24} \right) &= 125 \\ v_1 \left( -\frac{1}{6} \right) + v_2 \left( \frac{1}{6} + \frac{1}{2} + \frac{1}{12} \right) + v_3 \left( -\frac{1}{12} \right) &= 0 \\ v_1 \left( -\frac{1}{24} \right) + v_2 \left( -\frac{1}{12} \right) + v_3 \left( \frac{1}{1} + \frac{1}{12} + \frac{1}{24} \right) &= -125 \end{aligned}$$


Solving,  $v_1 = 101.24 \text{ V}$ ;  $v_2 = 10.66 \text{ V}$ ;  $v_3 = -106.57 \text{ V}$

$$\begin{aligned} \text{Thus, } i_1 &= \frac{125 - v_1}{1} = 23.76 \text{ A} & i_4 &= \frac{v_1 - v_2}{6} = 15.10 \text{ A} \\ i_2 &= \frac{v_2}{2} = 5.33 \text{ A} & i_5 &= \frac{v_2 - v_3}{12} = 9.77 \text{ A} \\ i_3 &= \frac{v_3 + 125}{1} = 18.43 \text{ A} & i_6 &= \frac{v_1 - v_3}{24} = 8.66 \text{ A} \end{aligned}$$

$$[\mathbf{b}] \sum P_{\text{dev}} = 125i_1 + 125i_3 = 5273.09 \text{ W}$$

$$\sum P_{\text{dis}} = i_1^2(1) + i_2^2(2) + i_3^2(1) + i_4^2(6) + i_5^2(12) + i_6^2(24) = 5273.09 \text{ W}$$

P 4.19

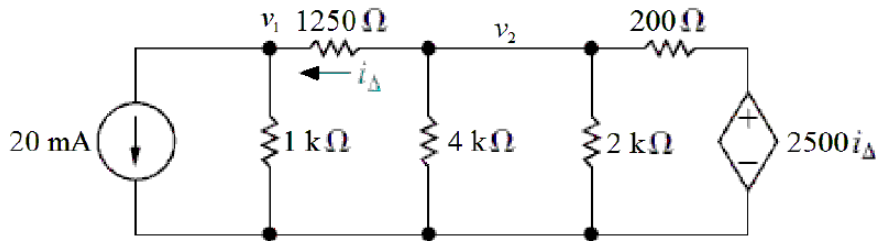

$$[\mathbf{a}] \quad 0.02 + \frac{v_1}{1000} + \frac{v_1 - v_2}{1250} = 0$$

$$\frac{v_2 - v_1}{1250} + \frac{v_2}{4000} + \frac{v_2}{2000} + \frac{v_2 - 2500i_{\Delta}}{200} = 0$$

$$i_{\Delta} = \frac{v_2 - v_1}{1250}$$

Solving,

$$v_1 = 60 \text{ V}; \quad v_2 = 160 \text{ V}; \quad i_{\Delta} = 80 \text{ mA}$$

$$P_{20\text{mA}} = (0.02)v_1 = (0.02)(60) = 1.2 \text{ W (absorbed)}$$

$$i_{\text{ds}} = \frac{v_2 - 2500i_{\Delta}}{200} = \frac{160 - (2500)(0.08)}{200} = -0.2 \text{ A}$$

$$P_{\text{ds}} = (2500i_{\Delta})i_{\text{ds}} = 2500(0.08)(-0.2) = -40 \text{ W (40 W developed)}$$

$$P_{\text{developed}} = 40 \text{ W}$$

$$[\text{b}] \quad P_{1\text{k}} = \frac{v_1^2}{1000} = \frac{60^2}{1000} = 3.6 \text{ W}$$

$$P_{1250} = 1250 i_{\Delta}^2 = 1250 (0.08)^2 = 8 \text{ W}$$


$$P_{4\text{k}} = \frac{v_2^2}{4000} = \frac{160^2}{4000} = 6.4 \text{ W}$$

$$P_{2\text{k}} = \frac{v_2^2}{2000} = \frac{160^2}{2000} = 12.8 \text{ W}$$

$$P_{200} = 200 i_{\text{ds}}^2 = 200 (-0.2)^2 = 8 \text{ W}$$

$$\begin{aligned} P_{\text{absorbed}} &= P_{20\text{mA}} + P_{1\text{k}} + P_{1250} + P_{4\text{k}} + P_{2\text{k}} + P_{200} \\ &= 1.2 + 3.6 + 8 + 6.4 + 12.8 + 8 = 40 \text{ W (check)} \end{aligned}$$

P 4.20

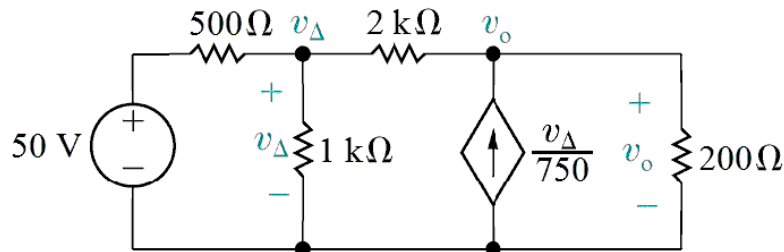

$$[\text{a}] \quad \frac{v_{\Delta} - 50}{500} + \frac{v_{\Delta}}{1000} + \frac{v_{\Delta} - v_o}{2000} = 0$$

$$\frac{v_o - v_{\Delta}}{2000} - \frac{v_{\Delta}}{750} + \frac{v_o}{200} = 0$$

Solving,

$$v_{\Delta} = 30 \text{ V}; \quad v_o = 10 \text{ V}$$

$$[\text{b}] \quad i_{50\text{V}} = \frac{v_{\Delta} - 50}{500} = \frac{30 - 50}{500} = -0.04 \text{ A}$$


$$P_{50\text{V}} = 50 i_{50\text{V}} = 50(-0.04) = -2 \text{ W} \quad (2 \text{ W supplied})$$

$$P_{\text{ds}} = -v_o \left( \frac{v_{\Delta}}{750} \right) = -(10)(30/750) = -0.4 \text{ W} \quad (0.4 \text{ W supplied})$$

$$P_{\text{total}} = 2 + 0.4 = 2.4 \text{ W supplied}$$

- P 4.54 [a] There are three unknown node voltages and only two unknown mesh currents. Use the mesh current method to minimize the number of simultaneous equations.

[b]

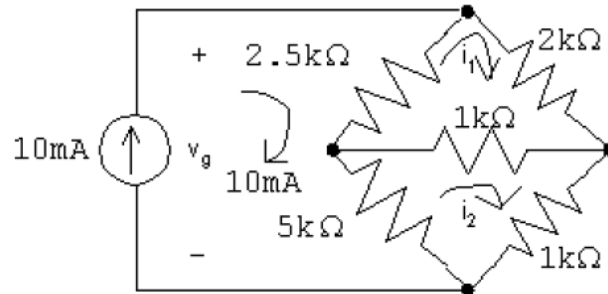

The mesh current equations:

$$2500(i_1 - 0.01) + 2000i_1 + 1000(i_1 - i_2) = 0$$

$$5000(i_2 - 0.01) + 1000(i_2 - i_1) + 1000i_2 = 0$$

Place the equations in standard form:

$$i_1(2500 + 2000 + 1000) + i_2(-1000) = 25$$

$$i_1(-1000) + i_2(5000 + 1000 + 1000) = 50$$

Solving,  $i_1 = 6 \text{ mA}$ ;  $i_2 = 8 \text{ mA}$


Find the power in the  $1 \text{ k}\Omega$  resistor:

$$i_{1k} = i_1 - i_2 = -2 \text{ mA}$$

$$p_{1k} = (-0.002)^2(1000) = 4 \text{ mW}$$

- [c] No, the voltage across the  $10 \text{ A}$  current source is readily available from the mesh currents, and solving two simultaneous mesh-current equations is less work than solving three node voltage equations.
- [d]  $v_g = 2000i_1 + 1000i_2 = 12 + 8 = 20 \text{ V}$   
 $p_{10\text{mA}} = -(20)(0.01) = -200 \text{ mW}$   
 Thus the  $10 \text{ mA}$  source develops  $200 \text{ mW}$ .

P 4.66

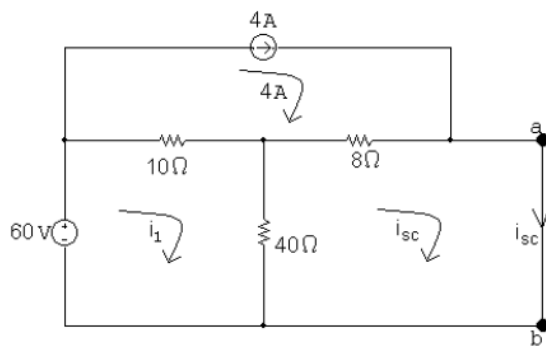


$$50i_1 - 40i_{sc} = 60 + 40$$


$$-40i_1 + 48i_{sc} = 32$$

Solving,  $i_{sc} = 7\text{ A}$
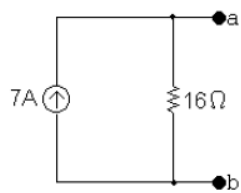
$$R_{Th} = 8 + \frac{(10)(40)}{50} = 16\ \Omega$$



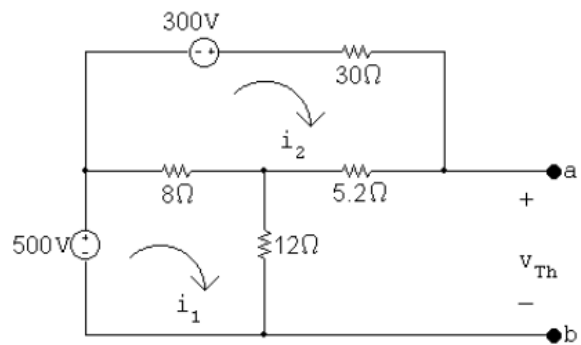P 4.67 After making a source transformation the circuit becomes



$$500 = 20i_1 - 8i_2$$

$$300 = -8i_1 + 43.2i_2$$

$$\therefore i_1 = 30 \text{ A and } i_2 = 12.5 \text{ A}$$

$$v_{Th} = 12i_1 + 5.2i_2 = 425 \text{ V}$$

$$R_{Th} = (8 \parallel 12 + 5.2) \parallel 30 = 7.5 \Omega$$

