

EEL 3112c – Circuits 2

Quiz on Chapter 9

Notes:

- Write your name on **all** pages
- Time limit is 20 minutes
- The quiz is closed book and closed notes
- You are allowed to use a calculator
- Show your work not just the final answer
- Your answers must be organized and easy to follow

Problem 1: (3 points)

Consider the sinusoidal voltage $v(t) = 40 \cos(200\pi t + 30^\circ)$

- a) What is the maximum amplitude of the voltage? (0.5 points)
- b) What is the frequency in hertz? (0.5 points)
- c) What is the frequency in rad/s? (0.5 points)
- d) What is the period in milliseconds? (0.5 points)
- e) What is the first time after $t = 0$ that $v = 0$ V? (0.5 points)
- f) What is the phasor representation (**V**) of $v(t)$? (0.5 points)

Solution:

- a) $V_m = 40$ V
- b) $2\pi f = 200\pi \rightarrow f = 100$ Hz
- c) $\omega = 200\pi = 628.318$ rad/s
- d) $T = \frac{1}{f} = \frac{1}{100} = 10$ ms
- e) $200\pi t + \frac{\pi}{6} = \frac{\pi}{2} \rightarrow 200\pi t = \frac{\pi}{3} \rightarrow t = \frac{1}{600} = 1.67$ ms
- f) $V = 40 \angle 30^\circ$

Problem 2: (2 points)

A 80 kHz sinusoidal voltage has zero phase angle and a maximum amplitude of 25 mV. When this voltage is applied across the terminals of a capacitor, the resulting steady-state current has a maximum amplitude of 628.32 μA .

- a) What is the frequency of the current in radians per second? (1 point)
- b) What is the phase angle of the current? (0.5 point)
- c) Using the phasor voltage and current, what is the impedance Z_c ? (1 point)

Solution:

a) $\omega = 2\pi f = 2\pi(80 \times 10^3) = 160\pi \times 10^3 = 502,654.82 \text{ rad/sec}$

b) In pure capacitive loads, the current leads the voltage

$$\theta_i = \theta_v + 90^\circ = 0 + 90 = 90^\circ$$

c) $Z_c = \frac{V}{I} = \frac{25 \times 10^{-3} \angle 0^\circ}{628.32 \times 10^{-6} \angle 90^\circ} = 39.79 \angle -90^\circ = -j39.79 \Omega$