

Ap 14.1 - 14.5 HW 7 Peter A. Dranishnikov

A14.1 Series RC lowpass filter requires a cutoff frequency of 8 kHz.

Use $R = 10 \text{ k}\Omega$ and compute the value of C required

$$2\pi \cdot f_c = \frac{1}{RC} \quad 2\pi \cdot 8000 = \frac{1}{10000C} \quad C = 1.989 \times 10^{-9} \text{ F}$$

A14.2 Series RL lowpass filter reqd. cutoff freq. of 2 kHz

Using $R = 5 \text{ k}\Omega$, compute

a) L

$$a) 2\pi f_c = \frac{R}{L}$$

b) $|H(j\omega)|$ at 50 kHz

$$2\pi 2000 = \frac{5000}{L}$$

c) $\theta(j\omega)$ at 50 kHz

$$b) |H(j\omega)| = \sqrt{\frac{R/L}{(\omega^2 + (R/L)^2}} = \sqrt{\frac{\frac{5000}{0.398}}{(2\pi 50000)^2 + \left(\frac{5000}{0.398}\right)^2}} = 0.040$$

$$c) \theta(j\omega) = -\tan^{-1} \left(\frac{50000 \cdot 2\pi \cdot 0.398}{5000} \right) \\ = -87.71^\circ$$

A14.3 Series RL hi pass $R = 5\text{k}\Omega$, $L = 3.5 \times 10^{-3}\text{H}$, what is ω_c ?

$$\omega_c = \frac{R}{L} = 1.43 \times 10^6 \text{ rad/s}$$

A14.4 Series RC Hi pass $C = 1 \times 10^{-6}\text{F}$,
cutoff freq. ω_c for

a) 100Ω d) $\frac{1}{RC} = \frac{1}{100 \cdot 10^{-6}} = 10000 \text{ rad/s}$

b) ~~5k\Omega~~

c) $30\text{k}\Omega$ b) $\frac{1}{5000 \cdot 10^{-6}} = 200 \text{ rad/s}$

c) $\frac{1}{30000 \cdot 10^{-6}} = 33.\bar{3} \text{ rad/s}$

A14.5 Compute the transfer function of a series RC lowpass filter w/ load resistor R_L in parallel w/ cap.

(unloaded) $\frac{R/L}{s + R/L}$

loaded

$$H(s) = \frac{\frac{R_L/sC}{R_L + sC}}{R + \frac{\frac{R_L/sC}{R_L + sC}}{R_L + sC}} = \frac{\frac{1}{RC}}{s + \frac{1}{KRC}}, K = \frac{R_L}{R + R_L}$$