

# **Chapter 6: Inductance, Capacitance, & Mutual Inductance**

**EEL 3112c – Circuits-II**


**Dr. Suleiman Alsweiss**

**ECE Department**

**Florida Polytechnic University**
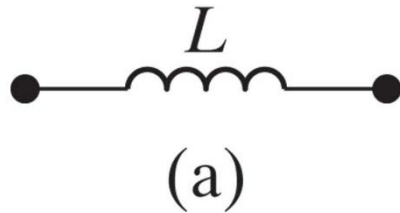
# The Inductor


- Inductance is the circuit parameter used to describe an inductor
- Inductance is symbolized by the letter  $L$ , is measured in henrys (**H**), and is represented graphically as a coil



- Assigning the reference direction of the current in the direction of the voltage drop across the terminals of the inductor, as shown in below, yields

The inductor  $v - i$  equation ►

$$v = L \frac{di}{dt},$$

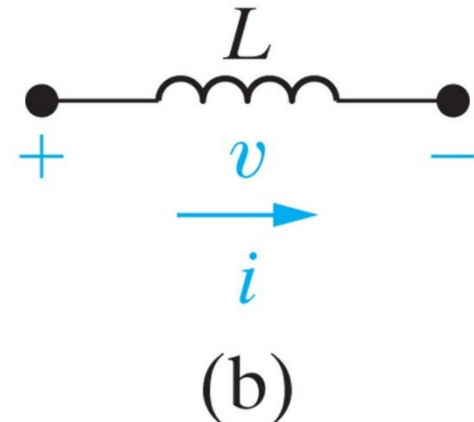

Where  $v$  is measured in volts,  $L$  in henrys,  $i$  in amperes, and  $t$  in seconds

# The Inductor – cont.

- Note from the inductor  $v - i$  equation, the voltage across the terminals of an inductor is proportional to the rate of change of the current in the inductor
- We can make two important observations here
  - First, if the current is constant, the voltage across the ideal inductor is zero
    - Thus the inductor behaves as a short circuit in the presence of a constant, or dc, current
  - Second, current cannot change instantaneously in an inductor; that is, the current cannot change by a finite amount in zero time
    - This change would require an infinite voltage, and infinite voltages are not possible

The instantaneous change is represented as a vertical line at the point of change, and the slope (i.e. derivative of a vertical line is infinity. Thus, instantaneous change in current will require infinite voltage which is not possible)

# Current in an Inductor in Terms of the Voltage Across the Inductor

$$\begin{aligned} v &= L \frac{di}{dt} \xrightarrow{\text{Integrate}} v dt = L di \xrightarrow{\text{Integrate}} L \int_{i(t_0)}^{i(t)} dx = \int_{t_0}^t v d\tau \\ &\downarrow \\ i(t) &= \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0) \xleftarrow{t_0 = 0} i(t) = \frac{1}{L} \int_0^t v d\tau + i(0) \end{aligned}$$

# Power and Energy in the Inductor

$$p = vi \rightarrow p = Li \frac{di}{dt} \quad \blacktriangleleft \text{Power in an inductor}$$


$$\rightarrow p = v \left[ \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0) \right].$$

$$p = \frac{dw}{dt} = Li \frac{di}{dt} \rightarrow dw = Li di \quad \textcolor{red}{w: \text{is energy in Joules}}$$

$$\int_0^w dx = L \int_0^i y dy \rightarrow w = \frac{1}{2} Li^2 \quad \blacktriangleleft \text{Energy in an inductor}$$
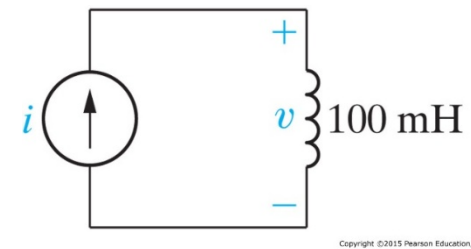
# Example 6.3


- The independent current source in the circuit shown below generates zero current for  $t < 0$  and a pulse  $10te^{-5t}$  A, for  $t > 0$  (Example 6.1)




$$i = 0, \quad t < 0$$

$$i = 10te^{-5t} \text{ A}, \quad t > 0$$


-ve slope leads to -ve voltage

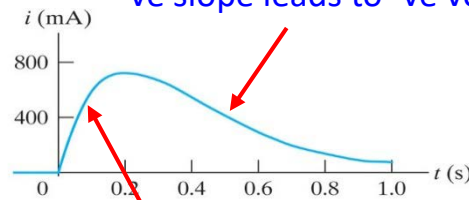


+ve slope leads to +ve voltage

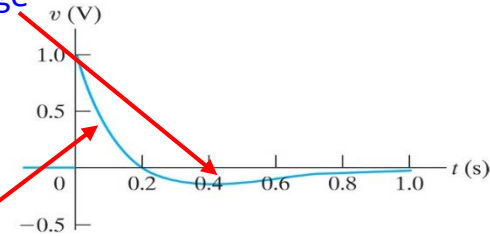

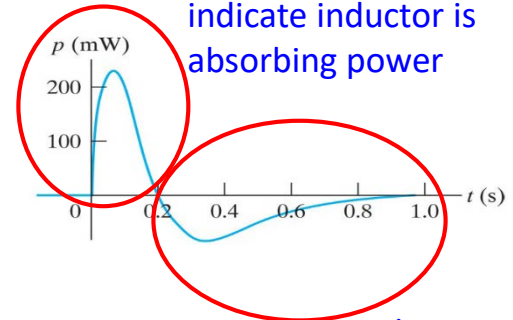+ve power to indicate inductor is absorbing power



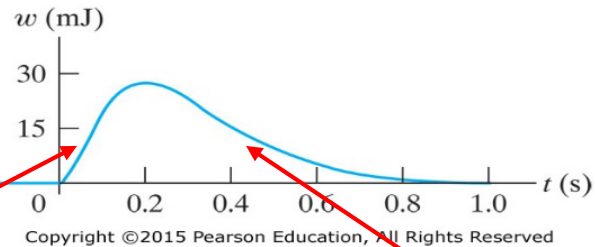-ve power to indicate inductor is generating power





An increasing energy curve indicates that energy is being stored. Note that this corresponds to the interval when  $p > 0$  (+ve power indicates the circuit element is absorbing power, thus the inductor is absorbing power by storing it)

A decreasing energy curve indicates that energy is being extracted. Note that this corresponds to the interval when  $p < 0$  (-ve power indicates the circuit element is generating power, thus the inductor is supplying back the power it stored previously)
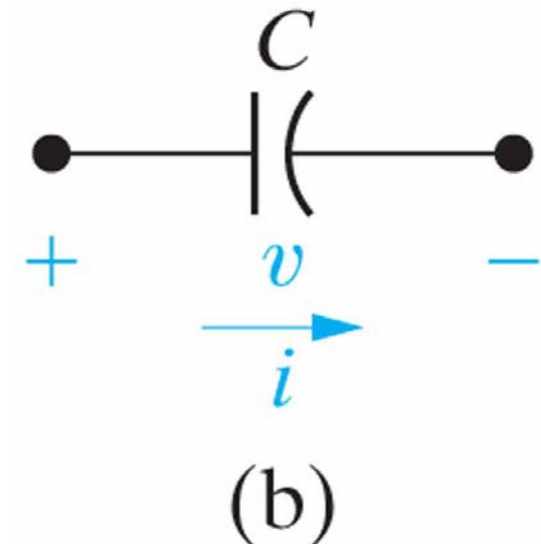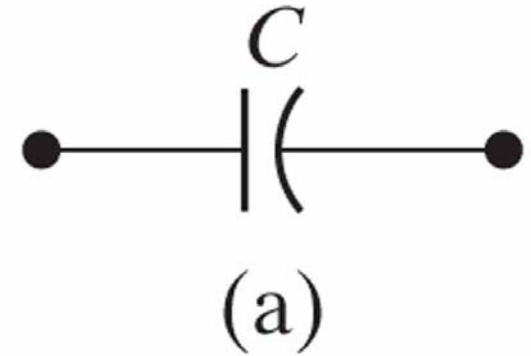
# The Capacitor

- The circuit parameter of capacitance
  - Represented by the letter  $C$
  - Measured in farads ( $F$ )
  - Symbolized graphically by two short parallel conductive plates
- Because the farad is an extremely large quantity of capacitance, practical capacitor values usually lie in the picofarad ( $pF$ ) to microfarad ( $\mu F$ ) range



# The Capacitor – cont.

- The graphic symbol for a capacitor is a reminder that capacitance occurs whenever electrical conductors are separated by a dielectric, or insulating, material
  - Dielectrics are very poor conductors
- This condition implies that electric charge is not transported through the capacitor
  - Although applying a voltage to the terminals of the capacitor cannot move a charge through the dielectric, it can displace a charge within the dielectric
  - As the voltage varies with time, the displacement of charge also varies with time, causing what is known as the **displacement current**



# The Capacitor – cont.

- The current is proportional to the rate at which the voltage across the capacitor varies with time

Capacitor  $i - v$  equation ►

$$i = C \frac{dv}{dt},$$

where  $i$  is measured in amperes,  $C$  in farads,  $v$  in volts, and  $t$  in seconds

- Two important observations follow from the capacitor  $i - v$  equation
  - First, if the voltage across the terminals is constant, the capacitor current is zero
    - Thus a capacitor behaves as an open circuit in the presence of a constant voltage
  - Second, voltage cannot change instantaneously across the terminals of a capacitor; that is, the voltage cannot change by a finite amount in zero time
    - Such a change would produce infinite current, a physical impossibility

# The Capacitor – cont.

- The capacitor  $i - v$  equation gives the capacitor current as a function of the capacitor voltage
- Expressing the voltage as a function of the current is also useful

The diagram illustrates the derivation of the capacitor voltage-current equation from the current-voltage equation. It starts with the equation  $i = C \frac{dv}{dt}$  in a light blue box. A blue arrow points to the differential equation  $i dt = C dv$ . A second blue arrow, labeled "Integrate" in red, points to the integrated form  $\int_{v(t_0)}^{v(t)} dx = \frac{1}{C} \int_{t_0}^t i d\tau$ . A vertical blue arrow points down to another light blue box containing  $v(t) = \frac{1}{C} \int_{t_0}^t i d\tau + v(t_0)$ , which is labeled "Capacitor  $v - i$  equation" with a red arrow. A final blue arrow, labeled "Let  $t_0 = 0$ " in red, points left to the equation  $v(t) = \frac{1}{C} \int_0^t i d\tau + v(0)$ .

$$i = C \frac{dv}{dt}, \quad \longrightarrow \quad i dt = C dv \quad \xrightarrow{\text{Integrate}} \quad \int_{v(t_0)}^{v(t)} dx = \frac{1}{C} \int_{t_0}^t i d\tau.$$
$$\downarrow$$
$$v(t) = \frac{1}{C} \int_{t_0}^t i d\tau + v(t_0). \quad \longleftarrow \text{Capacitor } v - i \text{ equation}$$
$$\xleftarrow{\text{Let } t_0 = 0} \quad v(t) = \frac{1}{C} \int_0^t i d\tau + v(0).$$

# Capacitor Energy & Power

$$p = vi = Cv \frac{dv}{dt},$$

(6.16) ◀ Capacitor power equation

$$w = \frac{1}{2}Cv^2.$$

(6.18) ◀ Capacitor energy equation


# Example 6.4:

The voltage pulse described by the following equations is impressed across the terminals of a  $0.5 \mu\text{F}$  capacitor:

$$v(t) = \begin{cases} 0, & t \leq 0 \text{ s}; \\ 4t \text{ V}, & 0 \text{ s} \leq t \leq 1 \text{ s}; \\ 4e^{-(t-1)} \text{ V}, & t \geq 1 \text{ s}. \end{cases}$$

An increasing energy curve indicates that energy is being stored. Note that this corresponds to the interval when  $p > 0$  (+ve power indicates the circuit element is absorbing power, thus the capacitor is absorbing power by storing it)

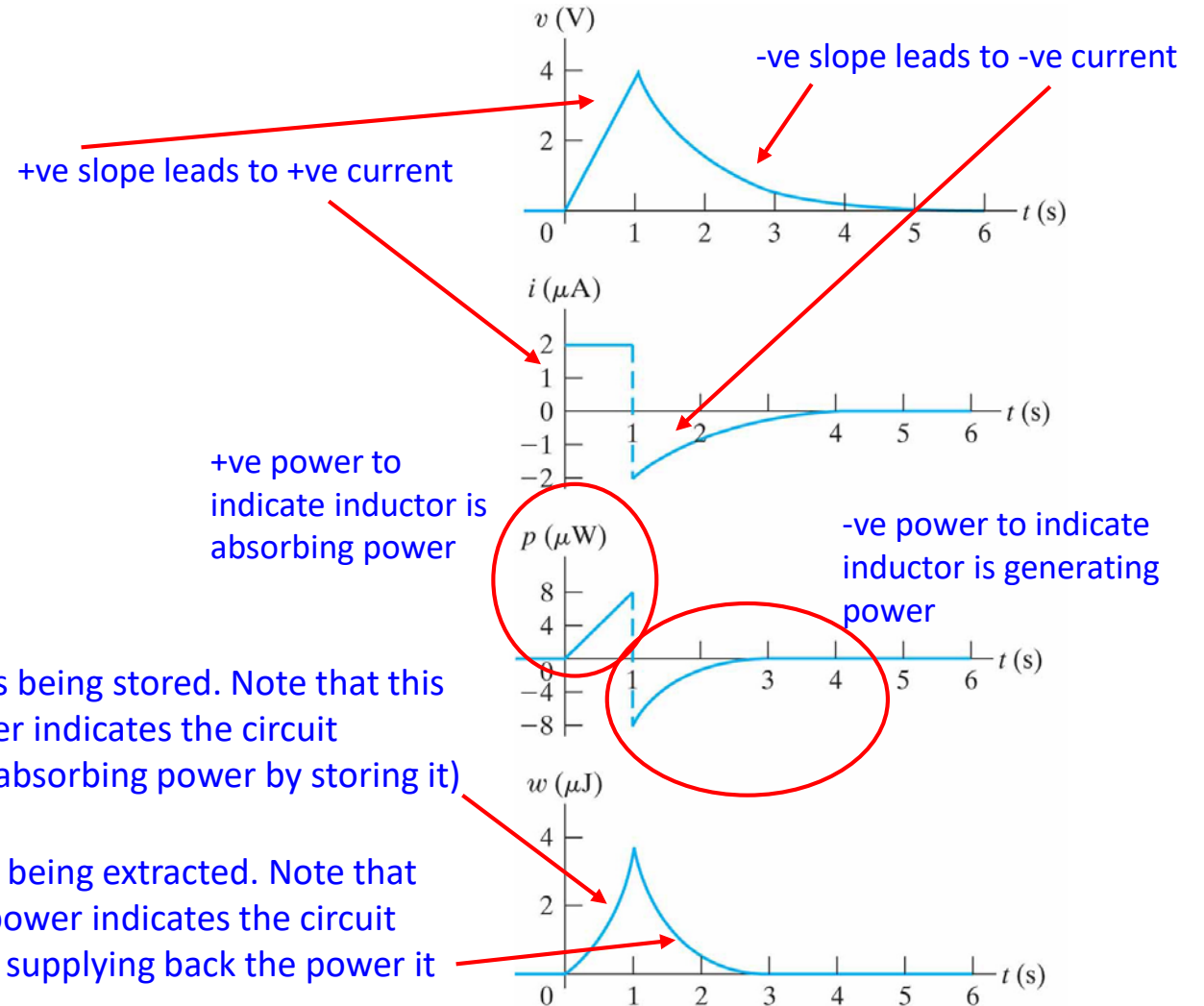
A decreasing energy curve indicates that energy is being extracted. Note that this corresponds to the interval when  $p < 0$  (-ve power indicates the circuit element is generating power, thus the capacitor is supplying back the power it stored previously)



# Series-Parallel Combinations of L & C


- Just as series-parallel combinations of resistors can be reduced to a single equivalent resistor, series-parallel combinations of inductors or capacitors can be reduced to a single inductor or capacitor
- **Elements connected in series are forced to carry the same current**
- **Elements connected in parallel are forced to have the same voltage**

# Inductors & Capacitors in Series

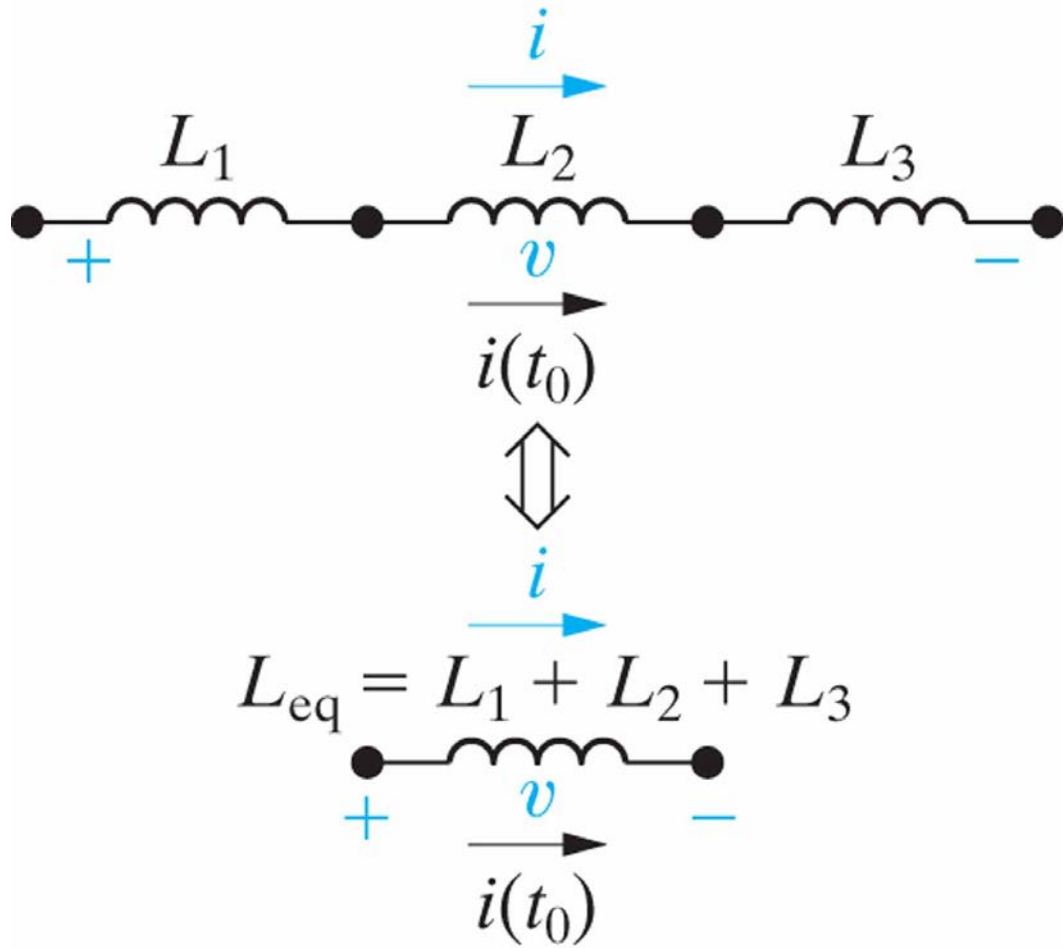


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall
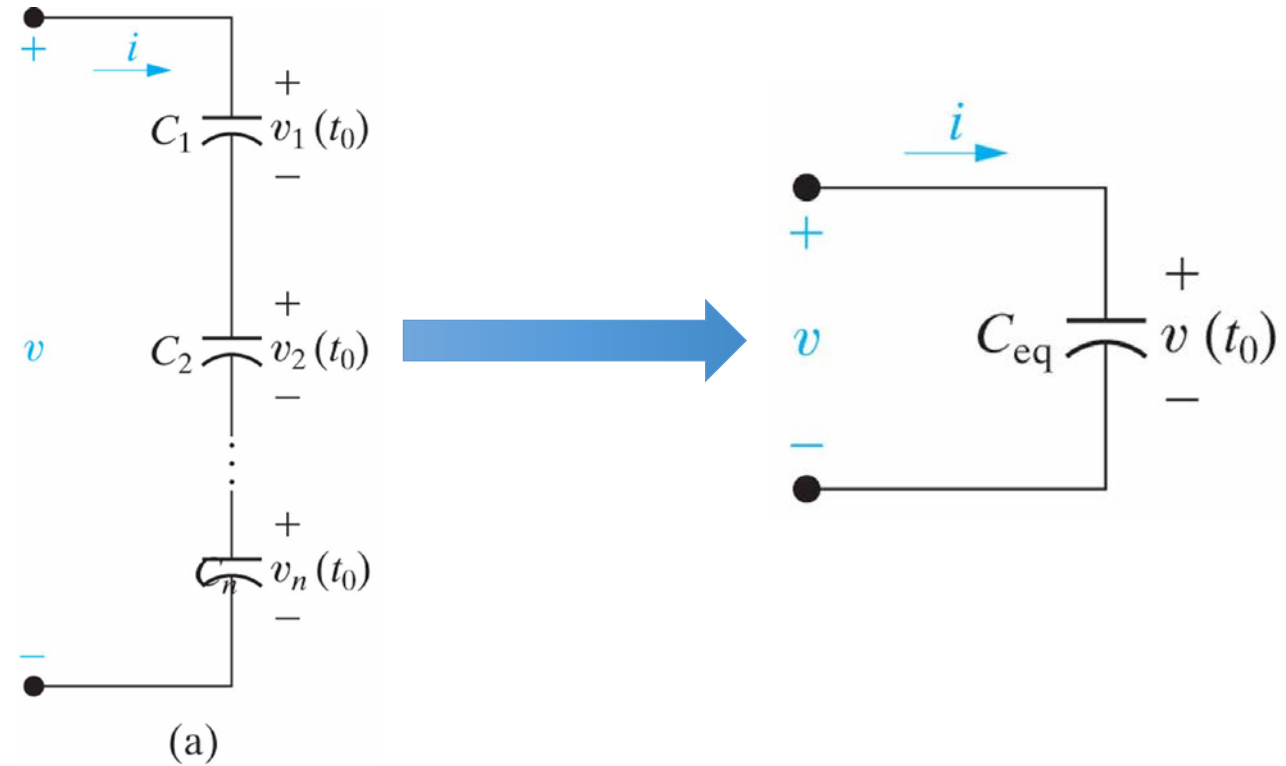
$$L_{eq} = L_1 + L_2 + L_3 + \cdots + L_n$$




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n}$$

# Inductors & Capacitors in Parallel

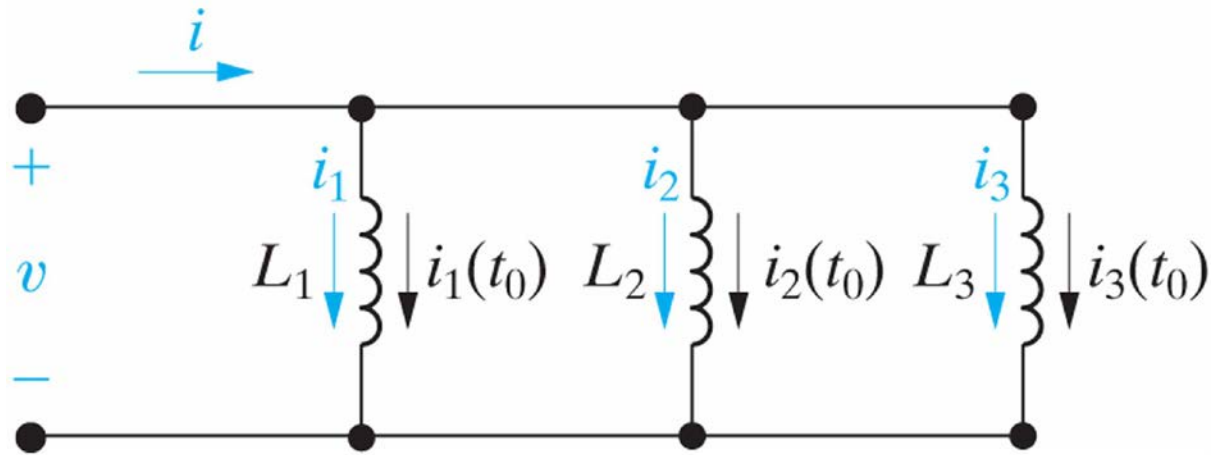


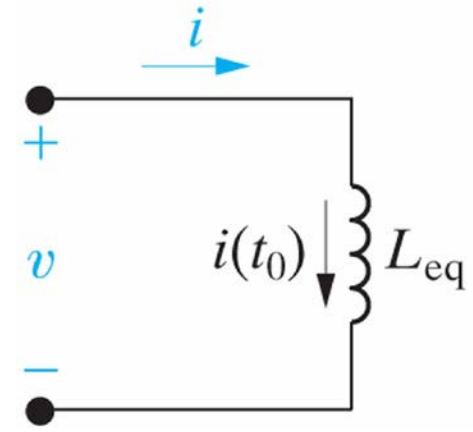Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall
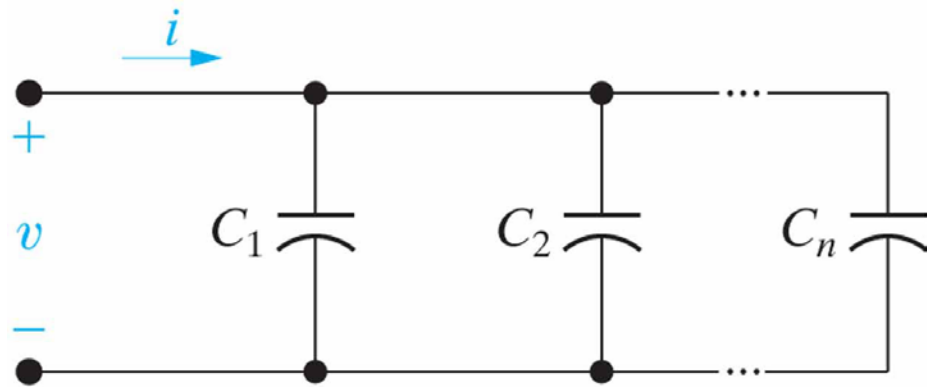
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$




Combining capacitors in parallel ►

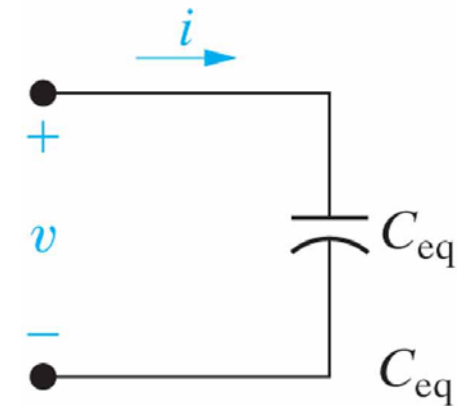

$$C_{eq} = C_1 + C_2 + \cdots + C_n$$
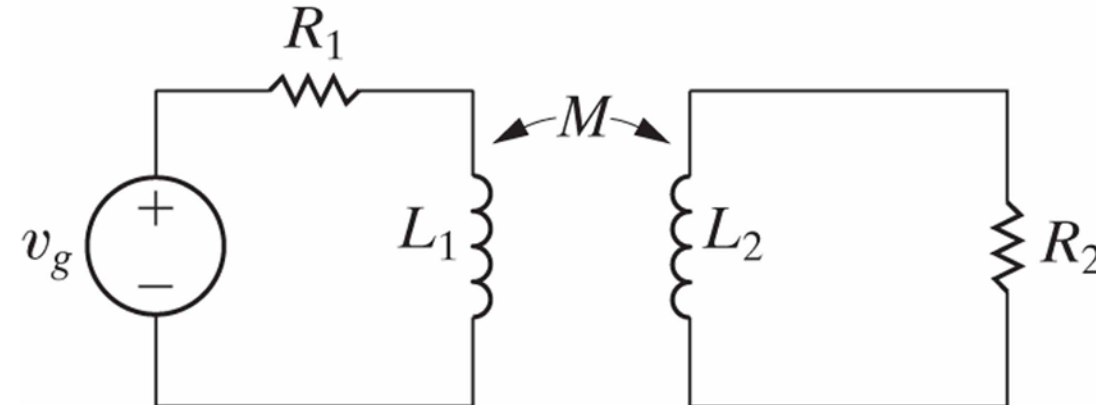
# Mutual Inductance


- We now consider the situation in which two circuits are linked by a magnetic field (magnetically coupled)
  - Any current flowing in a an inductor will generate a magnetic field
- In this case, the voltage induced in the second circuit can be related to the time-varying current in the first circuit by a parameter known as mutual inductance
  - The self-inductances of the two coils are labeled  $L_1$  and  $L_2$  and the mutual inductance is labeled  $M$
  - The double headed arrow adjacent to  $M$  indicates the pair of coils with this value of mutual inductance




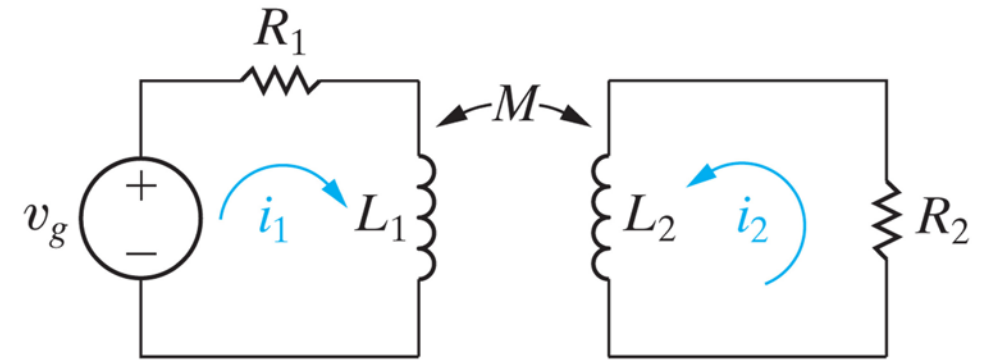
# Mutual Inductance – cont.

- The easiest way to analyze circuits containing mutual inductance is to use mesh currents
  - First select the reference direction for each coil
  - Then sum the voltages around each closed path
- Because of the mutual inductance  $M$ , there will be two voltages across each coil
  - Self-induced voltage
  - Mutually-induced voltage



## Left-hand circuit

Self-induced voltage:  $L_1 \frac{di_1}{dt}$


Mutually-induced voltage:  $M \frac{di_2}{dt}$

Note that the mutually induced voltage in one coil depends on the mutual inductance and the current of the other coil
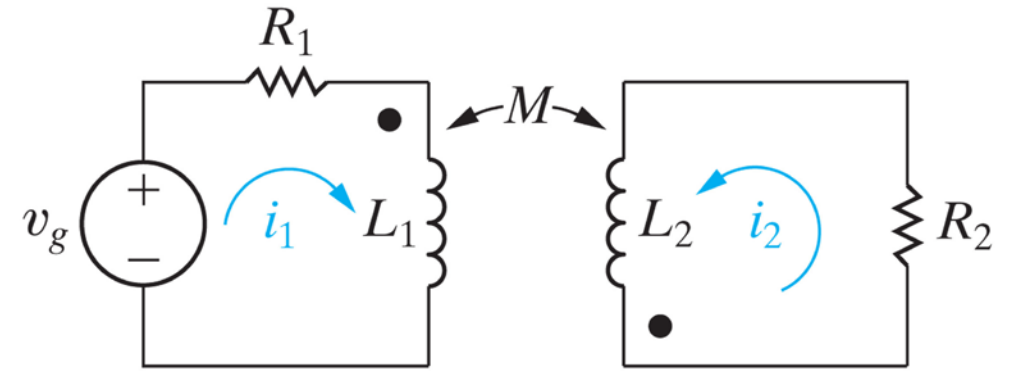
# Mutual Inductance – cont.

- Dot convention is used to determine polarity

- Dot is placed on one terminal of each winding
- These dots carry the sign information and allow us to draw the coils schematically rather than showing how they wrap around a core structure





- The rule for using the dot convention to determine the polarity of mutually induced voltage can be summarized as follows:

- When the reference direction for a current enters the dotted terminal of a coil, the reference polarity of the voltage that it induces in the other coil is positive at its dotted terminal

OR:

- When the reference direction for a current leaves the dotted terminal of a coil, the reference polarity of the voltage that it induces in the other coil is negative at its dotted terminal

# Mutual Inductance – cont.

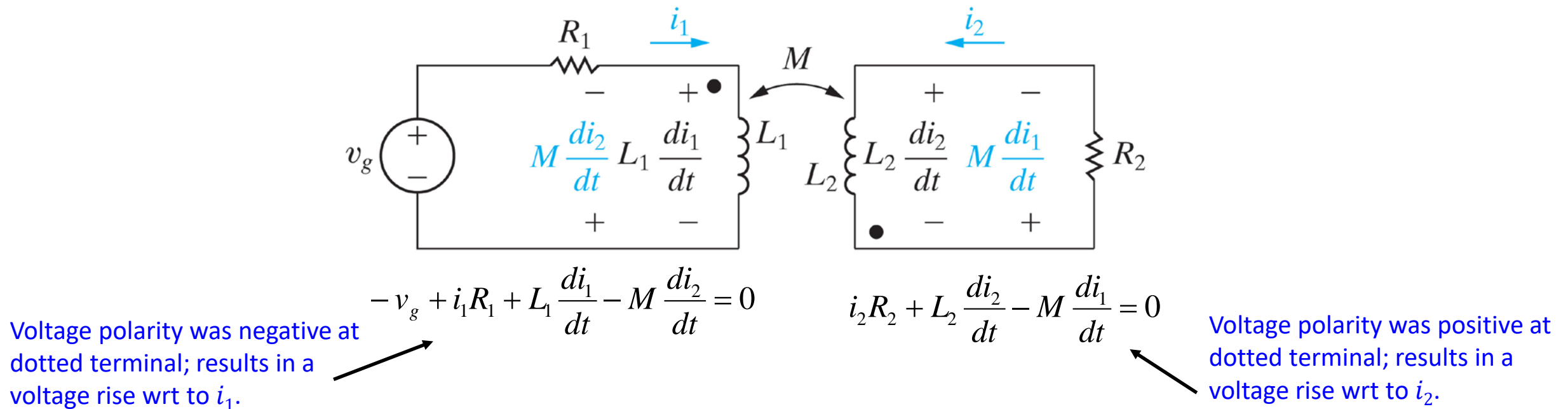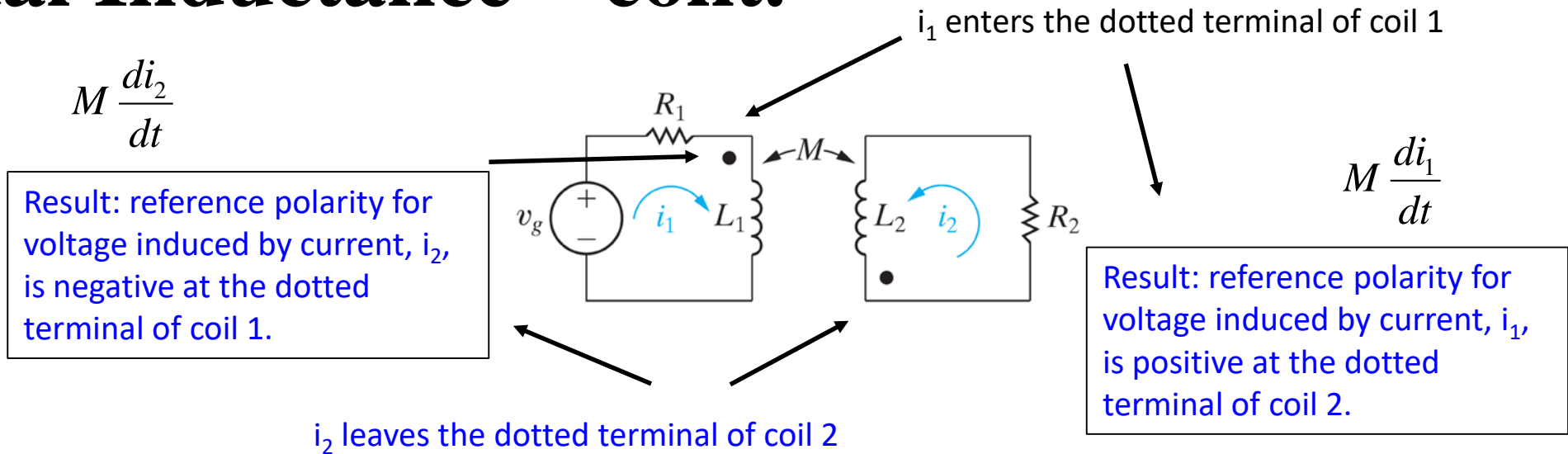

# Next Class

- Today we Reviewed Chapter 6
  - Inductance and capacitance
- Next class we will review chapter 7
  - Response of RL and RC circuits