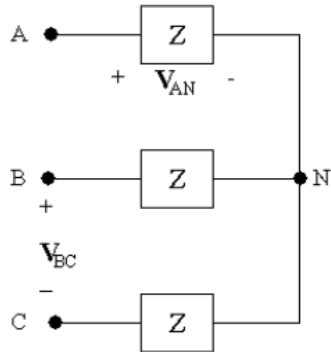


Circuits II

Ch11 Additional Problems Solution

AP 11.1 Make a sketch:



We know V_{AN} and wish to find V_{BC} . To do this, write a KVL equation to find V_{AB} , and use the known phase angle relationship between V_{AB} and V_{BC} to find V_{BC} .

$$V_{AB} = V_{AN} + V_{NB} = V_{AN} - V_{BN}$$

Since V_{AN} , V_{BN} , and V_{CN} form a balanced set, and $V_{AN} = 240/\underline{-30^\circ}\text{V}$, and the phase sequence is positive,

$$V_{BN} = |V_{AN}|/\underline{(\underline{V_{AN}} - 120^\circ)} = 240/\underline{-30^\circ - 120^\circ} = 240/\underline{-150^\circ}\text{V}$$

Then,

$$V_{AB} = V_{AN} - V_{BN} = (240/\underline{-30^\circ}) - (240/\underline{-150^\circ}) = 415.46/\underline{0^\circ}\text{V}$$


Since V_{AB} , V_{BC} , and V_{CA} form a balanced set with a positive phase sequence, we can find V_{BC} from V_{AB} :

$$V_{BC} = |V_{AB}|/\underline{(\underline{V_{AB}} - 120^\circ)} = 415.69/\underline{0^\circ - 120^\circ} = 415.69/\underline{-120^\circ}\text{V}$$

Thus,

$$V_{BC} = 415.69/\underline{-120^\circ}\text{V}$$

AP 11.2 Make a sketch:

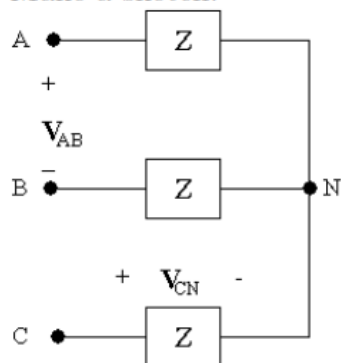

We know V_{CN} and wish to find V_{AB} . To do this, write a KVL equation to find V_{BC} , and use the known phase angle relationship between V_{AB} and V_{BC} to find V_{AB} .

$$V_{BC} = V_{BN} + V_{NC} = V_{BN} - V_{CN}$$

Since V_{AN} , V_{BN} , and V_{CN} form a balanced set, and $V_{CN} = 450/\underline{-25^\circ}$ V, and the phase sequence is negative,

$$V_{BN} = |V_{CN}|/\underline{\underline{V_{CN} - 120^\circ}} = 450/\underline{-25^\circ - 120^\circ} = 450/\underline{-145^\circ} \text{ V}$$

Then,

$$V_{BC} = V_{BN} - V_{CN} = (450/\underline{-145^\circ}) - (450/\underline{-25^\circ}) = 779.42/\underline{-175^\circ} \text{ V}$$


Since V_{AB} , V_{BC} , and V_{CA} form a balanced set with a negative phase sequence, we can find V_{AB} from V_{BC} :

$$V_{AB} = |V_{BC}|/\underline{\underline{V_{BC} - 120^\circ}} = 779.42/\underline{-295^\circ} \text{ V}$$

But we normally want phase angle values between $+180^\circ$ and -180° . We add 360° to the phase angle computed above. Thus,

$$V_{AB} = 779.42/\underline{65^\circ} \text{ V}$$

AP 11.3 Sketch the a-phase circuit:

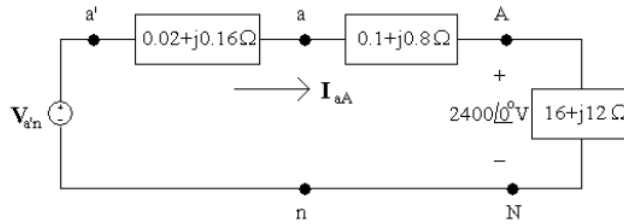

- [a] We can find the line current using Ohm's law, since the a-phase line current is the current in the a-phase load. Then we can use the fact that \mathbf{I}_{aA} , \mathbf{I}_{bB} , and \mathbf{I}_{cC} form a balanced set to find the remaining line currents. Note that since we were not given any phase angles in the problem statement, we can assume that the phase voltage given, \mathbf{V}_{AN} , has a phase angle of 0° .

$$2400\angle 0^\circ = \mathbf{I}_{aA}(16 + j12)$$

so

$$\mathbf{I}_{aA} = \frac{2400\angle 0^\circ}{16 + j12} = 96 - j72 = 120\angle -36.87^\circ \text{ A}$$

With an acb phase sequence,

$$\angle \mathbf{I}_{bB} = \angle \mathbf{I}_{aA} + 120^\circ \quad \text{and} \quad \angle \mathbf{I}_{cC} = \angle \mathbf{I}_{aA} - 120^\circ$$

so

$$\mathbf{I}_{aA} = 120\angle -36.87^\circ \text{ A}$$

$$\mathbf{I}_{bB} = 120\angle 83.13^\circ \text{ A}$$

$$\mathbf{I}_{cC} = 120\angle -156.87^\circ \text{ A}$$

- [b] The line voltages at the source are \mathbf{V}_{ab} , \mathbf{V}_{bc} , and \mathbf{V}_{ca} . They form a balanced set. To find \mathbf{V}_{ab} , use the a-phase circuit to find \mathbf{V}_{AN} , and use the relationship between phase voltages and line voltages for a y-connection (see Fig. 11.9[b]). From the a-phase circuit, use KVL:

$$\begin{aligned}\mathbf{V}_{an} &= \mathbf{V}_{aA} + \mathbf{V}_{AN} = (0.1 + j0.8)\mathbf{I}_{aA} + 2400/\underline{0^\circ} \\ &= (0.1 + j0.8)(96 - j72) + 2400/\underline{0^\circ} = 2467.2 + j69.6 \\ &\quad 2468.18/\underline{1.62^\circ} \text{ V}\end{aligned}$$

From Fig. 11.9(b),

$$\mathbf{V}_{ab} = \mathbf{V}_{an}(\sqrt{3}/\underline{-30^\circ}) = 4275.02/\underline{-28.38^\circ} \text{ V}$$

With an acb phase sequence,

$$\underline{\mathbf{V}_{bc}} = \underline{\mathbf{V}_{ab}} + 120^\circ \quad \text{and} \quad \underline{\mathbf{V}_{ca}} = \underline{\mathbf{V}_{ab}} - 120^\circ$$

so

$$\mathbf{V}_{ab} = 4275.02/\underline{-28.38^\circ} \text{ V}$$

$$\mathbf{V}_{bc} = 4275.02/\underline{91.62^\circ} \text{ V}$$

$$\mathbf{V}_{ca} = 4275.02/\underline{-148.38^\circ} \text{ V}$$

- [c] Using KVL on the a-phase circuit

$$\begin{aligned}\mathbf{V}_{a'n} &= \mathbf{V}_{a'A} + \mathbf{V}_{an} = (0.2 + j0.16)\mathbf{I}_{aA} + \mathbf{V}_{an} \\ &= (0.02 + j0.16)(96 - j72) + (2467.2 + j69.9) \\ &= 2480.64 + j83.52 = 2482.05/\underline{1.93^\circ} \text{ V}\end{aligned}$$

With an acb phase sequence,

$$\underline{\mathbf{V}_{b'n}} = \underline{\mathbf{V}_{a'n}} + 120^\circ \quad \text{and} \quad \underline{\mathbf{V}_{c'n}} = \underline{\mathbf{V}_{a'n}} - 120^\circ$$

so

$$\mathbf{V}_{a'n} = 2482.05/\underline{1.93^\circ} \text{ V}$$

$$\mathbf{V}_{b'n} = 2482.05/\underline{121.93^\circ} \text{ V}$$

$$\mathbf{V}_{c'n} = 2482.05/\underline{-118.07^\circ} \text{ V}$$

AP 11.4

$$\mathbf{I}_{cC} = (\sqrt{3}/\underline{-30^\circ})\mathbf{I}_{CA} = (\sqrt{3}/\underline{-30^\circ}) \cdot 8/\underline{-15^\circ} = 13.86/\underline{-45^\circ} \text{ A}$$

AP 11.5

$$\begin{aligned}\mathbf{I}_{aA} &= 12/(\underline{65^\circ - 120^\circ}) = 12/\underline{-55^\circ} \\ \mathbf{I}_{AB} &= \left[\left(\frac{1}{\sqrt{3}} \right) \underline{-30^\circ} \right] \mathbf{I}_{aA} = \left(\frac{\underline{-30^\circ}}{\sqrt{3}} \right) \cdot 12/\underline{-55^\circ} \\ &= 6.93/\underline{-85^\circ} \text{ A}\end{aligned}$$

AP 11.7

$$\mathbf{I}_\phi = \frac{110}{3.667} + \frac{110}{j2.75} = 30 - j40 = 50/\underline{-53.13^\circ} \text{ A}$$

$$\text{Therefore } |\mathbf{I}_{aA}| = \sqrt{3}\mathbf{I}_\phi = \sqrt{3}(50) = 86.60 \text{ A}$$

$$\text{AP 11.9 [a] } \mathbf{V}_{AN} = \left(\frac{2450}{\sqrt{3}} \right) \underline{0^\circ} \text{ V; } \quad \mathbf{V}_{AN}\mathbf{I}_{aA}^* = S_\phi = 144 + j192 \text{ kVA}$$

Therefore

$$\mathbf{I}_{aA}^* = \frac{(144 + j192)1000}{2450/\sqrt{3}} = (101.8 + j135.7) \text{ A}$$

$$\mathbf{I}_{aA} = 101.8 - j135.7 = 169.67/\underline{-53.13^\circ} \text{ A}$$

$$|\mathbf{I}_{aA}| = 169.67 \text{ A}$$

$$\text{[b] } P = \frac{(2450)^2}{R}; \quad \text{therefore } R = \frac{(2450)^2}{144,000} = 41.68 \, \Omega$$

$$Q = \frac{(2450)^2}{X}; \quad \text{therefore } X = \frac{(2450)^2}{192,000} = 31.26 \, \Omega$$

$$\text{[c] } Z_\phi = \frac{\mathbf{V}_{AN}}{\mathbf{I}_{aA}} = \frac{2450/\sqrt{3}}{169.67/\underline{-53.13^\circ}} = 8.34/\underline{53.13^\circ} = (5 + j6.67) \, \Omega$$

$$\therefore R = 5 \, \Omega, \quad X = 6.67 \, \Omega$$