

**EEL 3112C – Circuits-II****Fall 2019 First Exam****Important notes:**


- Write your **Full Name** on all pages
- Time limit is 50 minutes
- The exam is closed book and closed notes
- You are allowed to use a calculator
- **Always JUSTIFY your final answer and show relevant intermediate steps**
- Your answers must be organized and easy to follow
- If I cannot read or follow your answer, I will not grade it
- When answering different parts of a problem, please label them
- Always mention the unit for any physical quantity you find

Problem Number	Grade	Full Grade
Problem #1		40
Problem #2		30
Problem #3		30
<b>Total</b>		<b>100</b>

**Problem 1: (40 points)**

For the circuit shown below, the initial voltage across the 500 mH inductor is 15 V. The capacitor ( $C$ ) value is 40 nF, and the resistor ( $R$ ) equals 10 k $\Omega$ . Find the following:

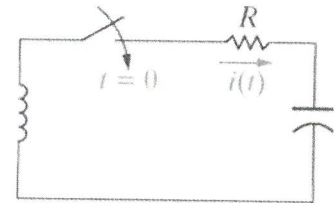- a) Find the roots of the characteristics equation that describes the natural behavior of the current  $i$  (i.e. find  $s_1$  &  $s_2$ )? (10 points)
- b) What type of damping describes the system and why? (10 points)
- c) Find the numerical values for  $i(0)$  and  $di(0)/dt$  immediately after the switch has been closed. (10 points)
- d)  $i(t)$  for  $t \geq 0$  (10 points)



# \* Problem 1:

1-1

⊛ For the series R, L, C circuit, we need to find:

a)  $S_1$  &  $S_2$ :

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \Rightarrow \alpha = \frac{R}{2L} = \frac{10 \times 10^3}{0.5} = 20,000 \text{ rad/s.}$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \omega_0^2 = \frac{1}{LC} = \frac{1}{0.5 (40 \times 10^{-9})} = 50 \times 10^6$$

$$\Rightarrow S_1 = -20,000 + \sqrt{(20,000)^2 - (50 \times 10^6)} = -1291.7$$

$$\Rightarrow S_2 = -20,000 - \sqrt{(20,000)^2 - (50 \times 10^6)} = -38708.3$$

b)  $\omega_0^2 < \alpha^2 \Rightarrow$  The system is overdamped.

c)  $i(0) = 0$ .

$$\frac{di(0)}{dt} = \frac{V_C(0)}{L} \rightarrow \text{@ } t=0, \text{ no current is passing through the circuit, } V_C(0) = V_L(0) = 15$$


$$\Rightarrow \frac{di(0)}{dt} = \frac{15}{0.5} = 30 \text{ A/s.}$$

$$d) i_1(t) = A_1 e^{-1291.7t} + A_2 e^{-38708.3t}$$

$$i(0) = A_1 + A_2 = 0, \quad \frac{di(0)}{dt} = -1291.7 A_1 - 38708.3 A_2 = 30$$

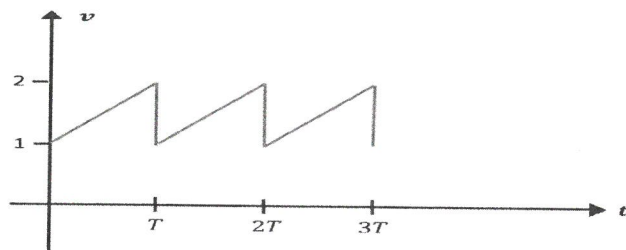**Problem 2: (30 points)**


Derive the expression for the RMS value of the following signal:


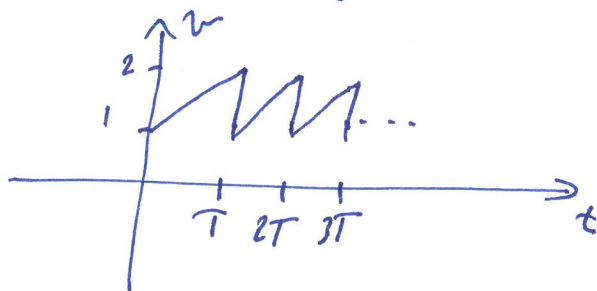
## \* Problem 2 :

2-1

We need to find the RMS value of the signal given in the plot.



① The period of this signal is  $T$ .

② The slope of this signal is :  $m = \frac{2-1}{T-0} = \frac{1}{T}$

③ The equation of the line between 0 &  $T$  is :  $v = \frac{1}{T}t + 1$

$$y = mx + b$$

④ Now, we have all what we need to find the RMS :

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{1}{T}t + 1\right)^2 dt}$$

$$v^2(t) = \left(\frac{1}{T}t + 1\right)^2 = \frac{1}{T^2}t^2 + \frac{2t}{T} + 1$$

$$\Rightarrow \int_0^T v^2(t) dt = \int_0^T \frac{1}{T^2}t^2 dt + \int_0^T \frac{2}{T}t dt + \int_0^T 1 dt$$


$$= \frac{1}{T^2} \left[ \frac{T^3}{3} \right] + \frac{2}{T} \frac{T^2}{2} + T$$

$$= \frac{T}{3} + T + T = \frac{7T}{3}$$

$$\Rightarrow V_{rms} = \sqrt{\frac{1}{T} \left[ \frac{7T}{3} \right]} = \boxed{\sqrt{\frac{7}{3}}} \#$$

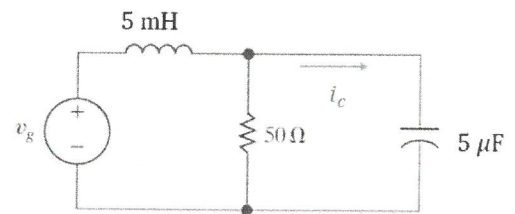**Problem 3: (30 points)**

The circuit shown below is operating in the sinusoidal steady state. Find the steady-state expression for  $i_c(t)$  if  $v_g = 50 \sin(2000t) \text{ V}$ .




### Problem 3:

3-1

② We need to find  $i_c(t)$  for the given circuit given that

$$v_g(t) = 50 \sin(2000t) \text{ V.}$$

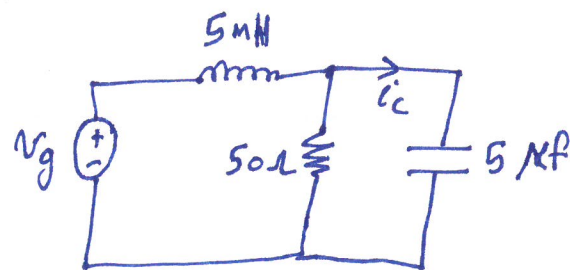

① First, we need to construct the frequency domain equivalent model:


- For the capacitor:  $\frac{1}{j\omega C} = \frac{1}{j(2000)(5 \times 10^{-6})} = \frac{1}{j(10^{-2})} = -j100$

- For the inductor:  $j\omega L = j(2000)(5 \times 10^{-3}) = j10$

-  $V_g = 50 \angle -90^\circ \text{ V.}$  ← note that we had to change the expression for  $v_g(t)$  from sin to cos

$$\Rightarrow v_g(t) = 50 \cos(2000t - 90^\circ) \text{ V.}$$

$\Rightarrow$

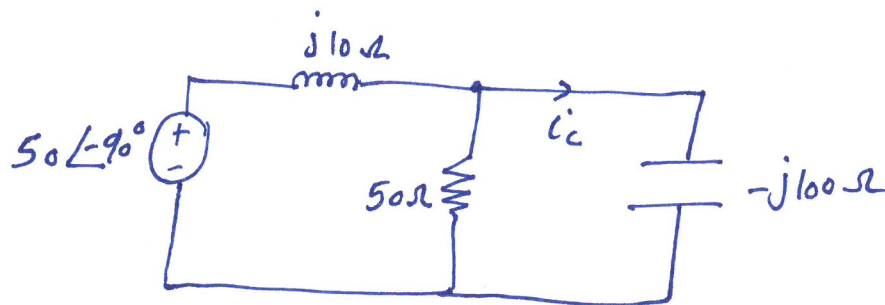

② To find  $i_c$ , we need to find the main current in the circuit & then use current divider.




### \* Problem 3 - Cont. :

3-2

Ⓐ To find the main current, we can simplify the circuit as follows:

$$Z_{eq} = j10 + (50 \parallel -j100)$$

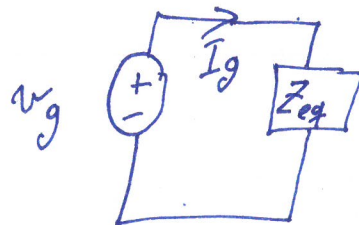

$$= j10 + \left( \frac{-j5000}{50 - j100} \right) = j10 + \left( \frac{5000 \angle -90^\circ}{111.8 \angle -63.4^\circ} \right)$$

$$= j10 + 44.7 \angle -26.6^\circ$$

$$\Rightarrow Z_{eq} = j10 + 39.97 - j20 = 39.97 - j10$$

$$\Rightarrow I_g = \frac{V_g}{Z_{eq}} = \frac{50 \angle -90^\circ}{41.2 \angle -14.04^\circ} = 1.21 \angle -75.96^\circ \text{ A.}$$

Ⓑ Now, to find  $i_c$  we can use current divider:

$$I_c = I_g \times \left( \frac{50}{50 - j100} \right) = I_g \times \left[ \frac{50 \angle 0^\circ}{111.8 \angle -63.4^\circ} \right]$$

$$I_c = I_g [0.4472 \angle 63.4^\circ] = (1.21 \angle -75.96^\circ)(0.4472 \angle 63.4^\circ)$$

$$\Rightarrow I_c = 0.5411 \angle -12.56^\circ \Rightarrow i_c(t) = 0.5411 \cos(2000t - 12.56^\circ) \text{ A.}$$

#