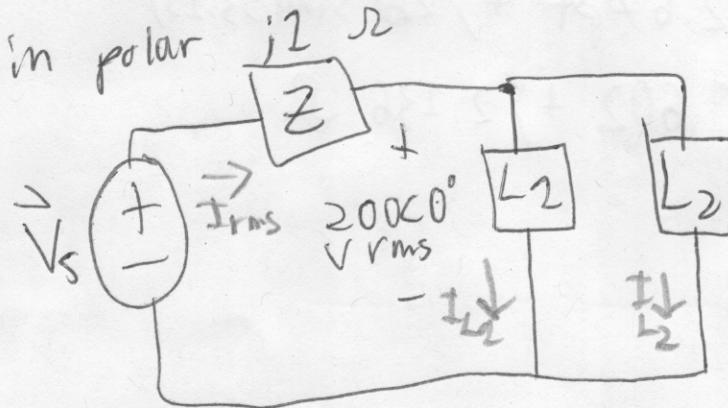


Peter A. Dranishnikov EEL 3212C

AP 10.6, 10.7
10.2, 10.28, 10.46

API 10.6 Find $V_{s\text{rms}}$ in circuit below if loads L_1, L_2

V_s in polar



15 kVA 6 kVA
0.6 pf -0.8 pf
(lag) (lead)

$$|S_{L_1}| = 15000 \text{ VA}$$

$$0.6 = \cos(\theta_v - \theta_i) \quad \theta_v - \theta_i = 53.13^\circ$$

$$|S_{L_2}| = 6000 \text{ VA}$$

$$-0.8 = \cos(\theta_v - \theta_i) \quad \theta_v - \theta_i = \frac{143.33^\circ}{36.87^\circ}$$

$$P_{L_1} = |S_{L_1}| \cos(\theta) = 15000 \cdot 0.6 = 9000 \text{ W}$$

$$Q_{L_1} = |S_{L_1}| \sin(\theta) = 15000 \cdot \sin(53.13) = 12000 \text{ VAR}$$

$$P_{L_2} = |S_{L_2}| \cos(\theta) = 6000 \cdot 0.8 = 4800 \text{ W}$$

$$Q_{L_2} = |S_{L_2}| \sin(\theta) = 6000 \cdot -0.6 = -3600 \text{ VAR}$$

$$S_{L_1} = 9000 + j12000 \text{ VA} \quad S_{L_1} + S_{L_2} = S = 13800 + j8400 \text{ VA}$$

$$S_{L_2} = 4800 - j3600 \text{ VA}$$

$$\theta = \tan^{-1}\left(\frac{8400}{13800}\right) = 31.33^\circ$$

$$\cos(\theta) = \text{pf} = 0.85 \text{ lag}$$

$$9000 = 200 |I_{eff}| 0.6$$

$$|I_{eff}| = 75 \text{ A}$$

$$|Z| = \frac{|V_{eff}|}{|I_{eff}|} = \frac{200}{75} = 2.67 \Omega$$

$$\begin{aligned} Z_1 &= 2.67 \angle 53.13^\circ = 2.67 \text{ pf} + j 2.67 \sin(53.13) \\ &= 1.602 + j 2.136 \Omega \end{aligned}$$

$$4800 = 200 |I_{eff}| 0.8$$

$$|I_{eff}| = 30 \text{ A}$$

$$|Z| = \frac{|V_{eff}|}{|I_{eff}|} = \frac{200}{30} = 6.67 \Omega$$

$$Z_2 = 6.67 \angle 36.87^\circ = 5.336 - j 4.00 \Omega$$

$$\vec{I}_1 = \frac{200}{1.602 + j 2.136} = 44.944 - j 59.93 \text{ A}$$

$$\vec{I}_2 = \frac{200}{5.336 - j 4} = 24.00 + j 17.99 \text{ A}$$


$$\vec{I}_1 + \vec{I}_2 = 68.94 - j 41.94 \text{ A} = \vec{I}$$

$$\vec{I} \cdot 1 = 41.94 + j 68.94 \text{ V}$$

$$\vec{V}_s = 41.94 + j 68.94 + 200 = 241.94 + j 68.94 \text{ V} = 251.57 \angle 15.91^\circ \text{ V}$$

AP 20.7

~~3 cos 5000t~~

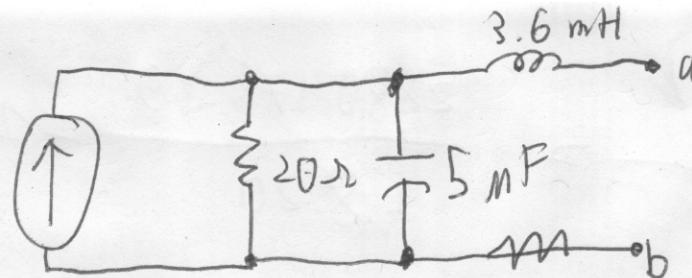




a) what impedance should be loaded for max avg power transfer?

b) What is average power transferred? ↑

c) Load must be pure resistance. What resistance loaded for max avg power transfer?

d) What is the average power transferred? ↑

e) $Z_{Th}^* = Z_L$

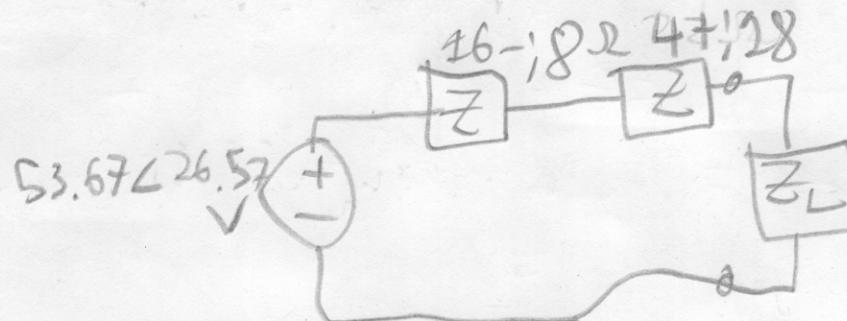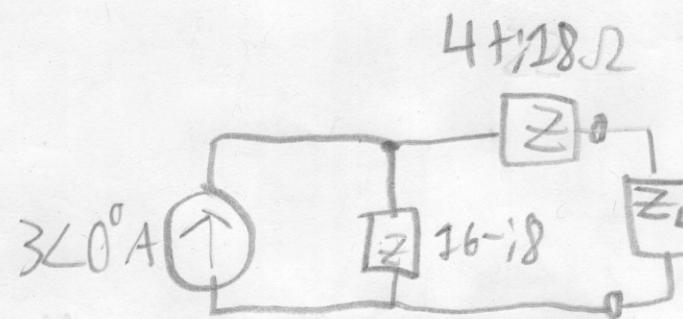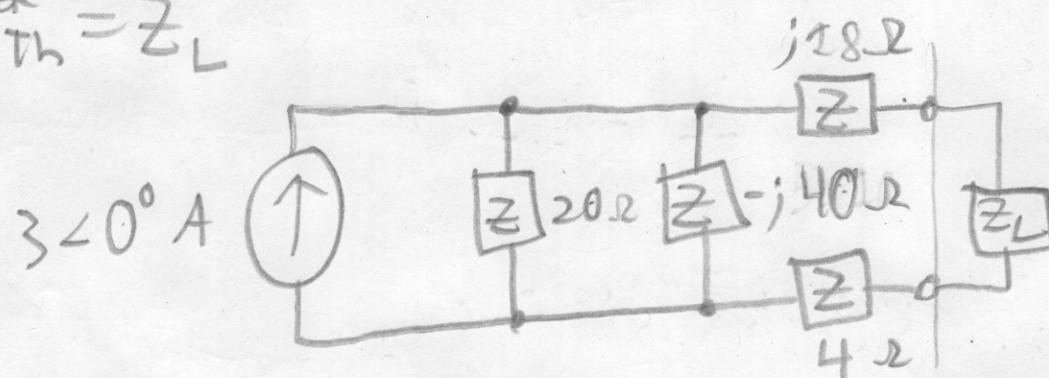

$$Z_{Th} = 20 + j10 \Omega$$

$$Z_{Th}^* = 20 - j20 \Omega$$

$$= Z_L$$

b)

$$\frac{|V_m|^2 R_{L\text{max}}}{8(R_R + R_L)} = \frac{2880.47 \cdot 20}{8 \cdot 20} = 18W$$

c)

$$\sqrt{R_{th}^2 + (0 + X_{th})^2} = \sqrt{20^2 + 10^2} = 22.36 \Omega = R_L$$

d)

$$\frac{|V_{rms}|^2 R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} = \frac{1440 \cdot 23 \cdot 22.36}{(20 + 22.36)^2 + 20^2} = 17W$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 37.95$$

20.2 a) TL; PR coffee maker, microwave, toaster, hot plate
in sum trip 50A Breaker on $120V_{rms}$ single phase?
b) add AC and Vacuum. Will it trip?

Too vague to answer tutor

coffee: ~~1200~~ power (avg) (W)

microwave: ~~2450~~

toaster: ~~2448~~ ~~2450~~

hot plate: ~~2246~~ ~~2196~~
~~2246~~

AC: ~~630~~ ~~860~~

Vacuum: ~~530~~ ~~2400~~

} d)

$$\begin{array}{r} 4992 \\ 5296 \end{array}$$

$$\begin{array}{r} 5296 \\ 4992 \\ \hline 120 \end{array} = 49.6 A$$

NO

NO

$$5296 + 5400 = 10696$$

$$\cancel{4992 + 2490} = 6482$$



b)

$$\begin{array}{r} 10696 \\ 6482 \\ \hline 120 \end{array} = \begin{array}{l} 89.13 A \\ 54.026 A \end{array}$$

YES

10.28 Find P, Q, |S| absorbed by load

$$150 \cos 250^\circ + j150 \text{ V}$$

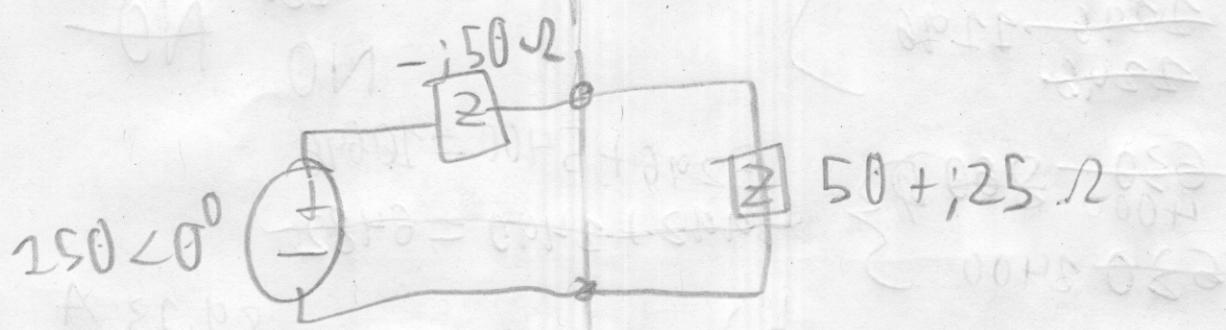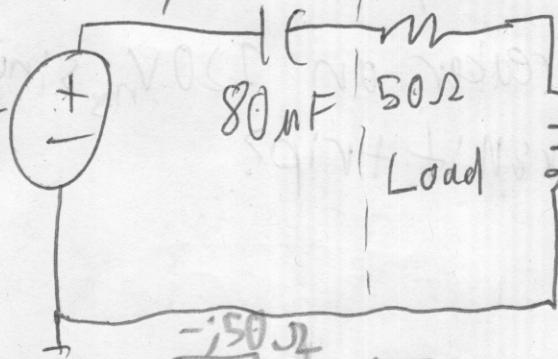

$$\frac{150}{\sqrt{2}} \text{ V}_{rms} = 106.07 \text{ V}$$

$$P = \frac{V_{rms}^2 \cdot R_L}{R_L^2 + (X_{Th} + X_L)^2} = \frac{(106.07)^2 \cdot 50}{50^2 + (-25)^2} = 180.01 \text{ W}$$

$$\frac{V_{rms}}{Z} = I_{rms} = \frac{106.07}{50 + j25} = 1.70 + j0.85 \text{ A} = 1.90 \angle -26.57^\circ \text{ A}$$

$$\frac{P}{V_{rms} I_{rms}} = pf = \frac{180.02}{106.07 \cdot 1.9} = 0.89 \text{ lagging} \quad \cos^{-1}(0.89) = 27.13^\circ$$

$$Q = |V_{rms}| |I_{rms}| \sin(27.13) = +91.90 \text{ VAR}$$


$$S = P + jQ = 180.01 + j91.90 \text{ VA} \quad |S| = 202.11 \text{ VA}$$

10.46 Varistor Var. resistor adjusted to max power




a) Find R

b) Find max avg power

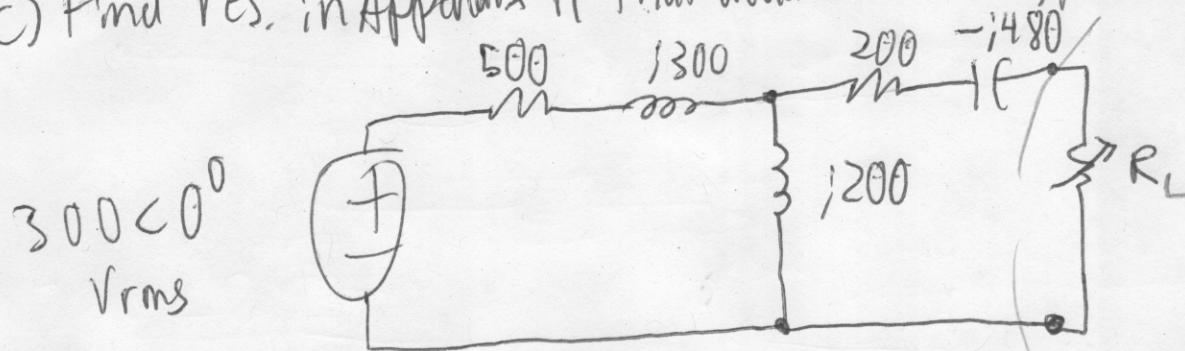c) Find res. in Appendix H that would have max avg power delivered



d)

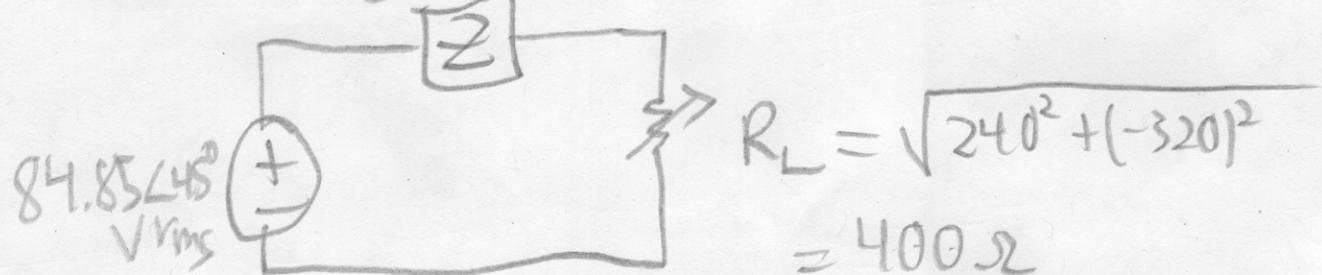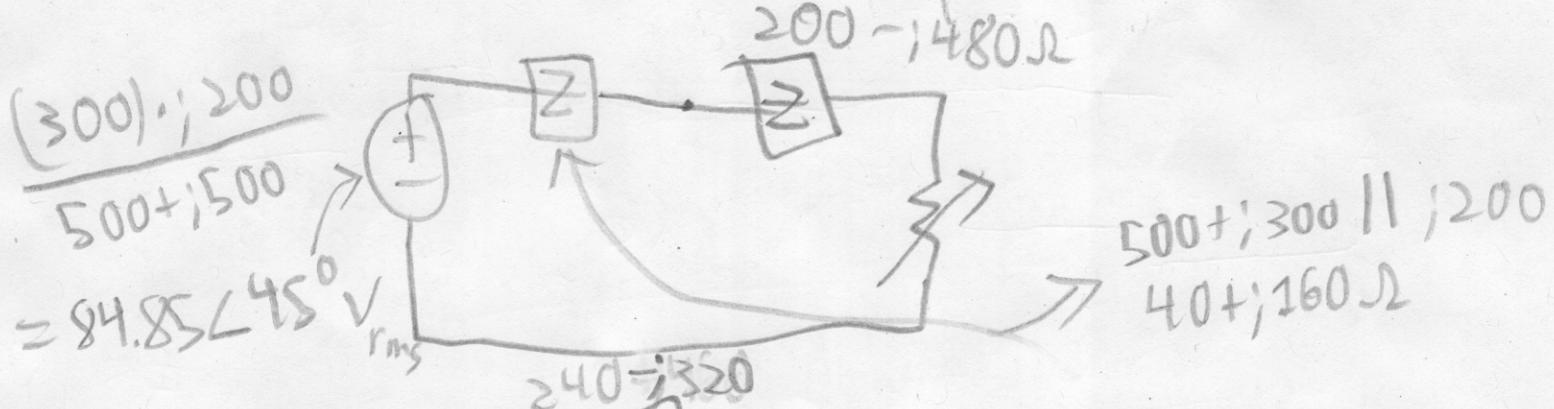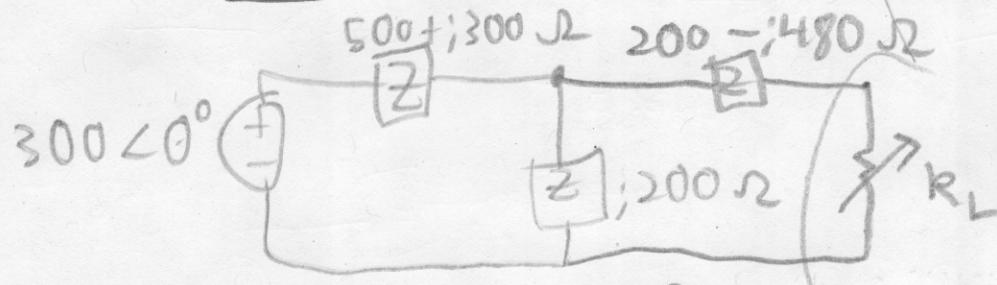

b) $\frac{|84.85|^2}{4 \cdot 400} = 4.50 \text{ W}$

c) 390 Ω nearest value