


Nominal	Actual
0.1 mF	0.09442 mF
20 mH	9.387 mH
1 k Ω	0.98230 k Ω
50 Ω	51.375 Ω

Simulator results (src 1 & 2)

$$E_1 = 1.1188 \text{ V}_{\text{rms}}$$

$$E_2 = 1.0546 \text{ V}_{\text{eff}}$$

$$V_R = 1.1170 \text{ V}_p$$

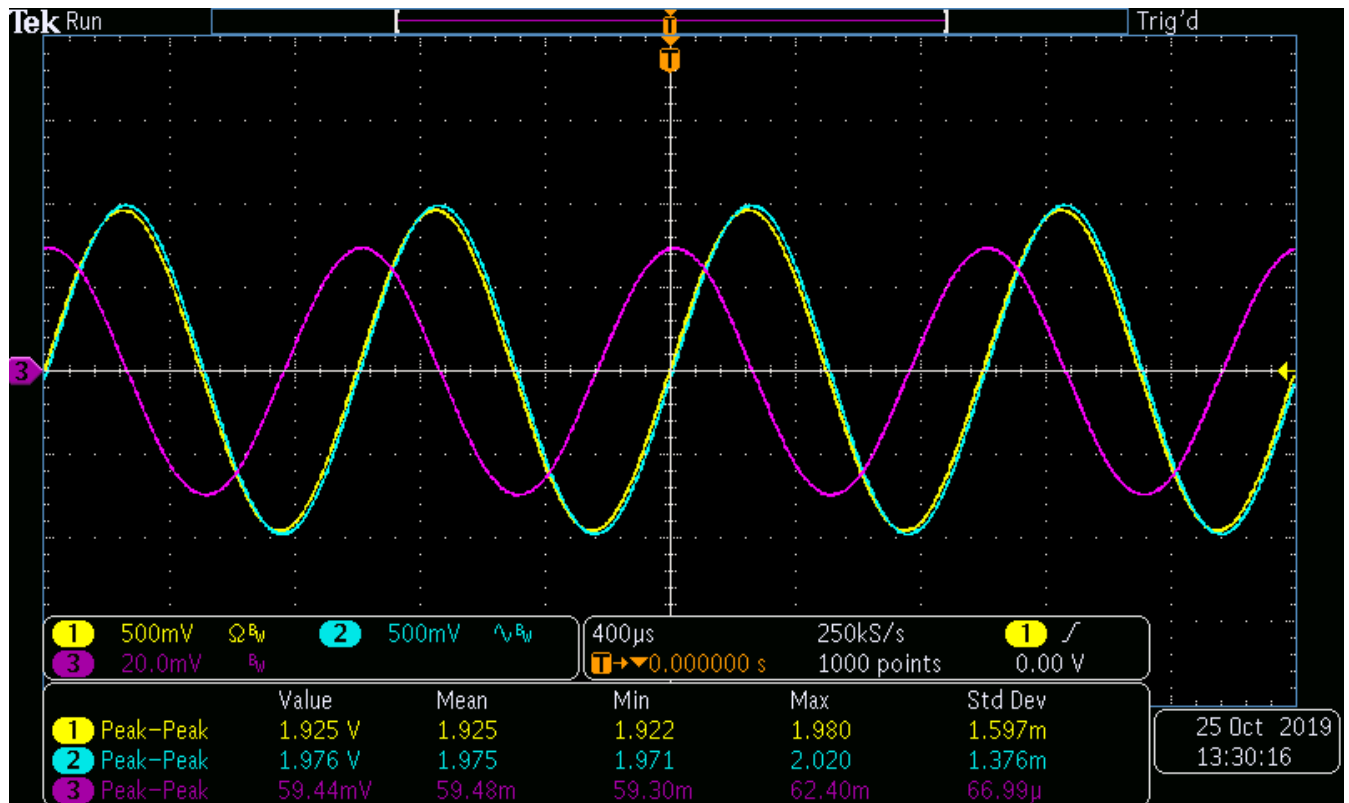

25 Oct 2019
13:30:16

Data Tables

Source One Only

V_{PP}

	Theory	Experimental	% Deviation
E_1	2	1.925 V_{PP}	3.75
E_2	0.06301	1.975 V_{PP} 0.05946 V_{PP}	5.63
V_R	2.0683	1.975 V_{PP}	4.52

Table 10.1

Source Two Only


	Theory	Experimental	% Deviation
E_1	0.1736	0.2243 V_{PP}	29.24
E_2	2	1.856 V_{PP}	7.20
V_R	2.693	2.526 V_{PP}	6.19

Table 10.2

Sources One and Two

	Theory	Experimental	% Deviation
E_1	2	1.898 V_{PP}	5.10
E_2	2	2.000 V_{PP}	0
V_R	2.3805	1.945 V_{PP}	18.29

Table 10.3

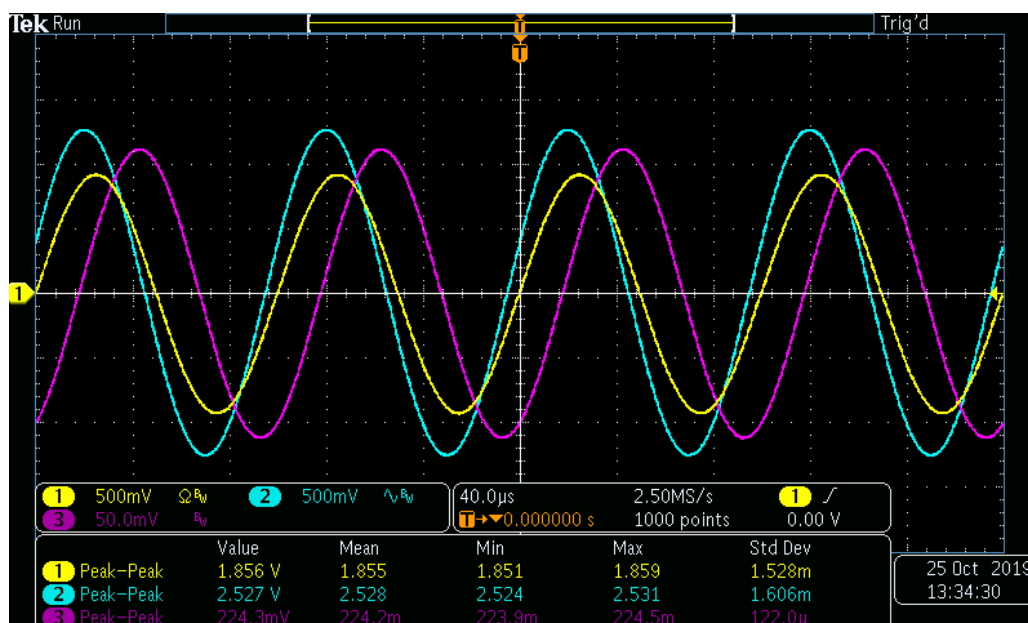

Questions

1. Why must the sources be replaced with a $50\ \Omega$ resistor instead of being shorted?


The loading impedance of the AC source is $50\ \Omega$, thus for accurate superposition calculations.


2. Do the expected maxima and minima from step 6 match what is measured in step 7?

Yes

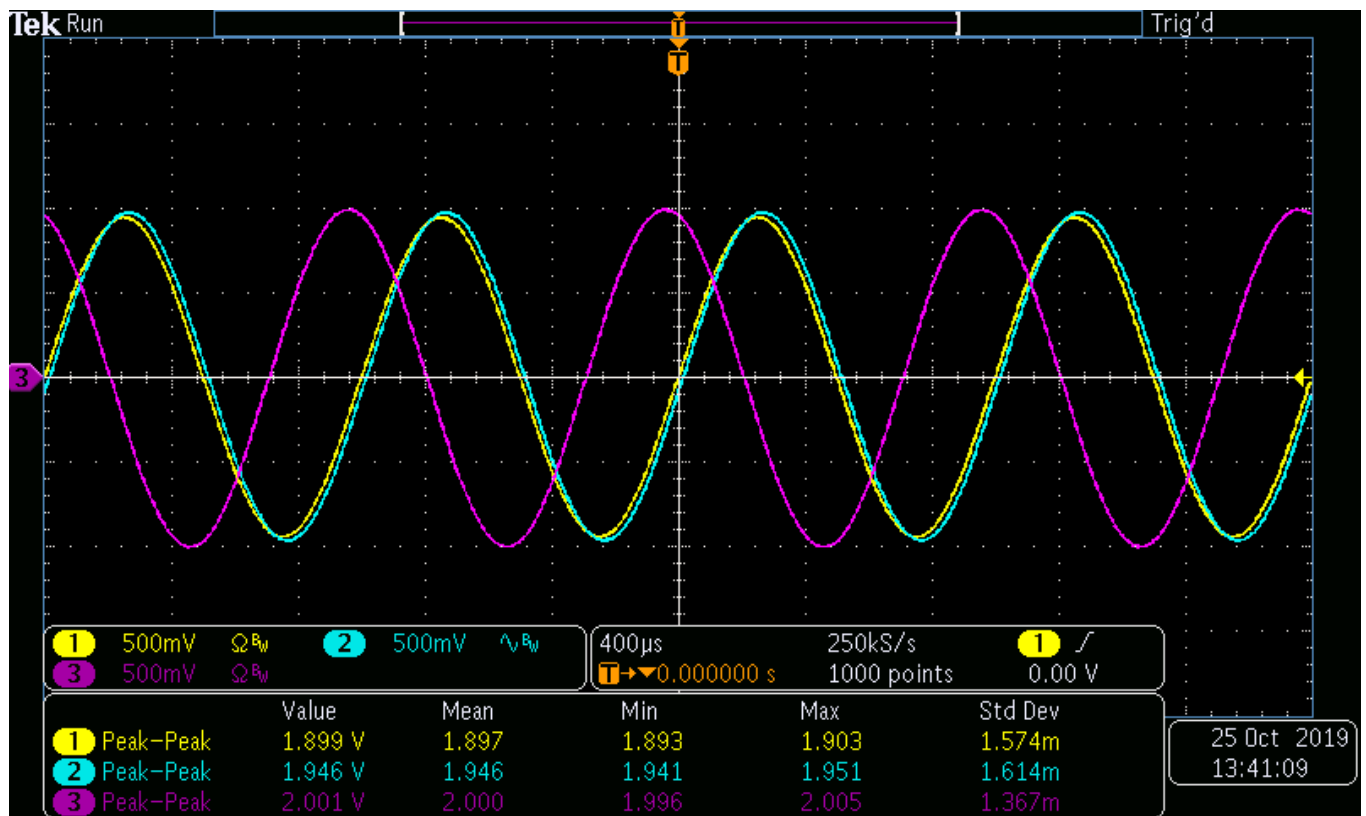3. Does one source tend to dominate the $1\ \text{k}\Omega$ resistor voltage or do both sources contribute in nearly equal amounts? Will this always be the case?

There is a slight domination due to the differing capacitor and inductor impedances. If the sources were out of phase, then a clear domination wld occur depending on the phase angle amount.



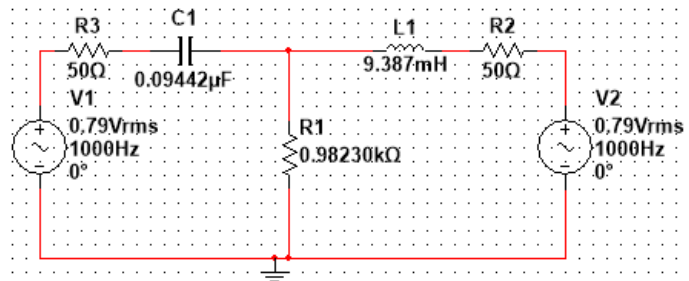

Cursor			
	V(1)	V(2)	V(3)
x1	6.2471m	6.2471m	6.2471m
y1	1.1188	1.0546	1.1170
x2	4.2471m	4.2471m	4.2471m
y2	1.1188	1.0546	1.1170
dx	-2.0000m	-2.0000m	-2.0000m
dy	-2.2204e-016	-8.8818e-016	-2.2204e-016
dy/dx	1.1102e-013	4.4409e-013	1.1102e-013
1/dx	-500.0000	-500.0000	-500.0000

