

Circuits II

Home Work # 4 (Ch11) Solution

$$\text{AP 11.6 [a] } \mathbf{I}_{AB} = \left[\left(\frac{1}{\sqrt{3}} \right) \angle 30^\circ \right] [69.28 \angle -10^\circ] = 40 \angle 20^\circ \text{ A}$$

$$\text{Therefore } Z_\phi = \frac{4160 \angle 0^\circ}{40 \angle 20^\circ} = 104 \angle -20^\circ \Omega$$

$$\text{[b] } \mathbf{I}_{AB} = \left[\left(\frac{1}{\sqrt{3}} \right) \angle -30^\circ \right] [69.28 \angle -10^\circ] = 40 \angle -40^\circ \text{ A}$$

$$\text{Therefore } Z_\phi = 104 \angle 40^\circ \Omega$$

$$\text{AP 11.8 [a] } |S| = \sqrt{3}(208)(73.8) = 26,587.67 \text{ VA}$$

$$Q = \sqrt{(26,587.67)^2 - (22,659)^2} = 13,909.50 \text{ VAR}$$

$$\text{[b] pf} = \frac{22,659}{26,587.67} = 0.8522 \quad \text{lagging}$$

P 11.1 [a] First, convert the cosine waveforms to phasors:

$$\mathbf{V}_a = 137/\underline{63^\circ}; \quad \mathbf{V}_b = 137/\underline{-57^\circ}; \quad \mathbf{V}_c = 137/\underline{183^\circ}$$

Subtract the phase angle of the a-phase from all phase angles:

$$\underline{V}'_a = 63^\circ - 63^\circ = 0^\circ$$

$$\underline{V}'_b = -57^\circ - 63^\circ = -120^\circ$$

$$\underline{V}'_c = 183^\circ - 63^\circ = 120^\circ$$

Compare the result to Eqs. 11.1 and 11.2:

Therefore abc

[b] First, convert the cosine waveforms to phasors, making sure that all waveforms are represented as cosines:

$$\mathbf{V}_a = 820/\underline{-36^\circ}; \quad \mathbf{V}_b = 820/\underline{84^\circ}; \quad \mathbf{V}_c = 820/\underline{-156^\circ}$$

Subtract the phase angle of the a-phase from all phase angles:

$$\underline{V}'_a = -36^\circ + 36^\circ = 0^\circ$$

$$\underline{V}'_b = 84^\circ + 36^\circ = 120^\circ$$

$$\underline{V}'_c = -156^\circ + 36^\circ = -120^\circ$$

Compare the result to Eqs. 11.1 and 11.2:

Therefore acb

P 11.8 $Z_{ga} + Z_{la} + Z_{La} = 60 + j80 \Omega$

$$Z_{gb} + Z_{lb} + Z_{Lb} = 90 + j120 \Omega$$

$$Z_{gc} + Z_{lc} + Z_{Lc} = 30 + j40 \Omega$$


$$\frac{\mathbf{V}_N - 320}{60 + j80} + \frac{\mathbf{V}_N - 320/\underline{-120^\circ}}{90 + j120} + \frac{\mathbf{V}_N - 320/\underline{120^\circ}}{30 + j40} + \frac{\mathbf{V}_N}{20} = 0$$

Solving for \mathbf{V}_N yields

$$\mathbf{V}_N = 49.47/\underline{75.14^\circ} \text{ V (rms)}$$

$$\mathbf{I}_o = \frac{\mathbf{V}_N}{20} = 2.47/\underline{75.14^\circ} \text{ A (rms)}$$

P 11.12 Make a sketch of the a-phase:

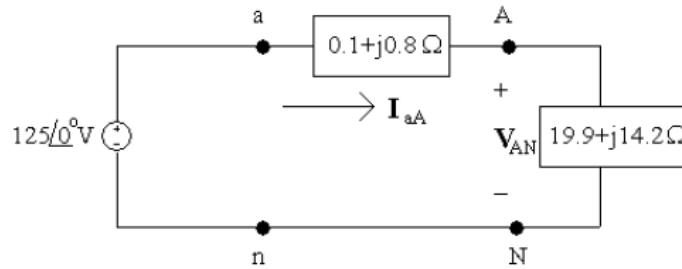

[a] Find the a-phase line current from the a-phase circuit:

$$\begin{aligned} \mathbf{I}_{aA} &= \frac{125/0^\circ}{0.1 + j0.8 + 19.9 + j14.2} = \frac{125/0^\circ}{20 + j15} \\ &= 4 - j3 = 5 \angle -36.87^\circ \text{ A (rms)} \end{aligned}$$

Find the other line currents using the acb phase sequence:

$$\mathbf{I}_{bB} = 5 \angle -36.87^\circ + 120^\circ = 5 \angle 83.13^\circ \text{ A (rms)}$$

$$\mathbf{I}_{cC} = 5 \angle -36.87^\circ - 120^\circ = 5 \angle -156.87^\circ \text{ A (rms)}$$

[b] The phase voltage at the source is $\mathbf{V}_{an} = 125 \angle 0^\circ$ V. Use Fig. 11.9(b) to find the line voltage, \mathbf{V}_{ab} , from the phase voltage:

$$\mathbf{V}_{ab} = \mathbf{V}_{an}(\sqrt{3} \angle -30^\circ) = 216.51 \angle -30^\circ \text{ V (rms)}$$

Find the other line voltages using the acb phase sequence:

$$\mathbf{V}_{bc} = 216.51 \angle -30^\circ + 120^\circ = 216.51 \angle 90^\circ \text{ V (rms)}$$

$$\mathbf{V}_{ca} = 216.51 \angle -30^\circ - 120^\circ = 216.51 \angle -150^\circ \text{ V (rms)}$$

[c] The phase voltage at the load in the a-phase is \mathbf{V}_{AN} . Calculate its value using \mathbf{I}_{aA} and the load impedance:

$$\mathbf{V}_{AN} = \mathbf{I}_{aA} Z_L = (4 - j3)(19.9 + j14.2) = 122.2 - j2.9 = 122.23 \angle -1.36^\circ \text{ V (rms)}$$

Find the phase voltage at the load for the b- and c-phases using the acb sequence:

$$\mathbf{V}_{BN} = 122.23 \angle -1.36^\circ + 120^\circ = 122.23 \angle 118.64^\circ \text{ V (rms)}$$

$$\mathbf{V}_{CN} = 122.23 \angle -1.36^\circ - 120^\circ = 122.23 \angle -121.36^\circ \text{ V (rms)}$$

- [d] The line voltage at the load in the a-phase is V_{AB} . Find this line voltage from the phase voltage at the load in the a-phase, V_{AN} , using Fig. 11.9(b):

$$V_{AB} = V_{AN}(\sqrt{3}/-30^\circ) = 211.72/-31.36^\circ \text{ V (rms)}$$

Find the line voltage at the load for the b- and c-phases using the acb sequence:


$$V_{BC} = 211.72/-31.36^\circ + 120^\circ = 211.72/88.64^\circ \text{ V (rms)}$$

$$V_{CA} = 211.72/-31.36^\circ - 120^\circ = 211.72/-151.36^\circ \text{ V (rms)}$$

P 11.37 [a] $S_{g/\phi} = \frac{1}{3}(41.6)(0.707 + j0.707) \times 10^3 = 9803.73 + j9803.73 \text{ VA}$

$$I_{aA}^* = \frac{9803.73 + j9803.73}{240/\sqrt{3}} = 70.76 + j70.76 \text{ A (rms)}$$
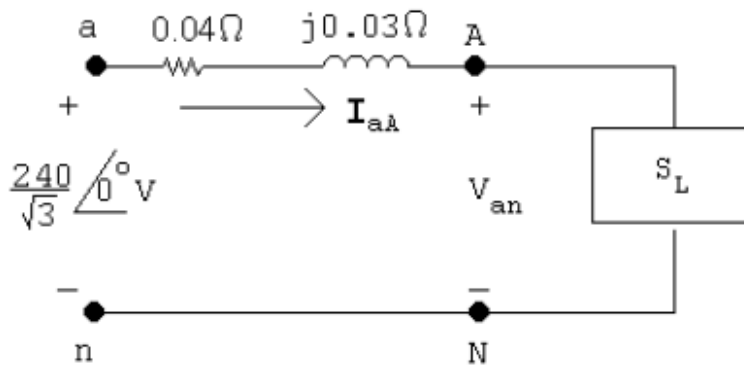
$$I_{aA} = 70.76 - j70.76 \text{ A (rms)}$$



$$\begin{aligned} V_{AN} &= \frac{240}{\sqrt{3}} - (0.04 + j0.03)(70.76 - j70.76) \\ &= 133.61 + j0.71 = 133.61/0.30^\circ \text{ V (rms)} \end{aligned}$$

$$|V_{AB}| = \sqrt{3}(133.61) = 231.42 \text{ V (rms)}$$

$$[\mathbf{b}] \ S_{L/\phi} = (133.61 + j0.71)(70.76 + j70.76) = 9404 + j9504.5 \text{ VA}$$

$$S_L = 3S_{L/\phi} = 28,212 + j28,513 \text{ VA}$$

Check:

$$S_g = 41,600(0.7071 + j0.7071) = 29,415 + j29,415 \text{ VA}$$

$$P_\ell = 3|\mathbf{I}_{aA}|^2(0.04) = 1202 \text{ W}$$

$$P_g = P_L + P_\ell = 28,212 + 1202 = 29,414 \text{ W} \quad (\text{checks})$$

$$Q_\ell = 3|\mathbf{I}_{aA}|^2(0.03) = 901 \text{ VAR}$$

$$Q_g = Q_L + Q_\ell = 28,513 + 901 = 29,414 \text{ VAR} \quad (\text{checks})$$