

# **AC Maximum Power Transfer**

## **EEL 3112C – Circuits-II**

### **Lab Experiment**

**Dr. Suleiman Alsweiss**

**ECE Department**

**Florida Polytechnic University**

# Objective

- In this exercise, maximum power transfer to the load will be examined for the AC case
- Both the load's resistive and reactive components will be independently varied to discover their effect of load power and determine the values required for maximum load power

# Theory Overview

- In the DC case, maximum power transfer is achieved by setting the load resistance equal to the Thevenin equivalent resistance
- For the AC case, the load should be set to complex conjugate of the Thevenin equivalent impedance ( $\mathbf{Z_L = Z_{Th}^*}$ )
  - The complex conjugate having the same magnitude as the original but with the opposite sign for the angle
  - By using the complex conjugate, the load and source reactive components will cancel out leaving a purely resistive circuit similar to the DC case
  - When calculating the true load power average power, only the real part of the load impedance dissipates power

$$P_{max} = |I_{Th_{rms}}|^2 R_L = \frac{|V_{Th_{rms}}|^2 R_L}{4R_L^2} = \frac{1}{8} \frac{V_{peak}^2}{R_L}$$

# Components

Component name	Quantity	Value	Measured value
Resistors	2	1 K $\Omega$	
	1	3 K $\Omega$	
	1	10 K $\Omega$	
	1	100 $\Omega$	
	1	600 $\Omega$	
Inductor	1	10 mH	
Capacitor	4	0.1 $\mu F$	
	1	10 nF	
	1	47 nF	

# Schematics

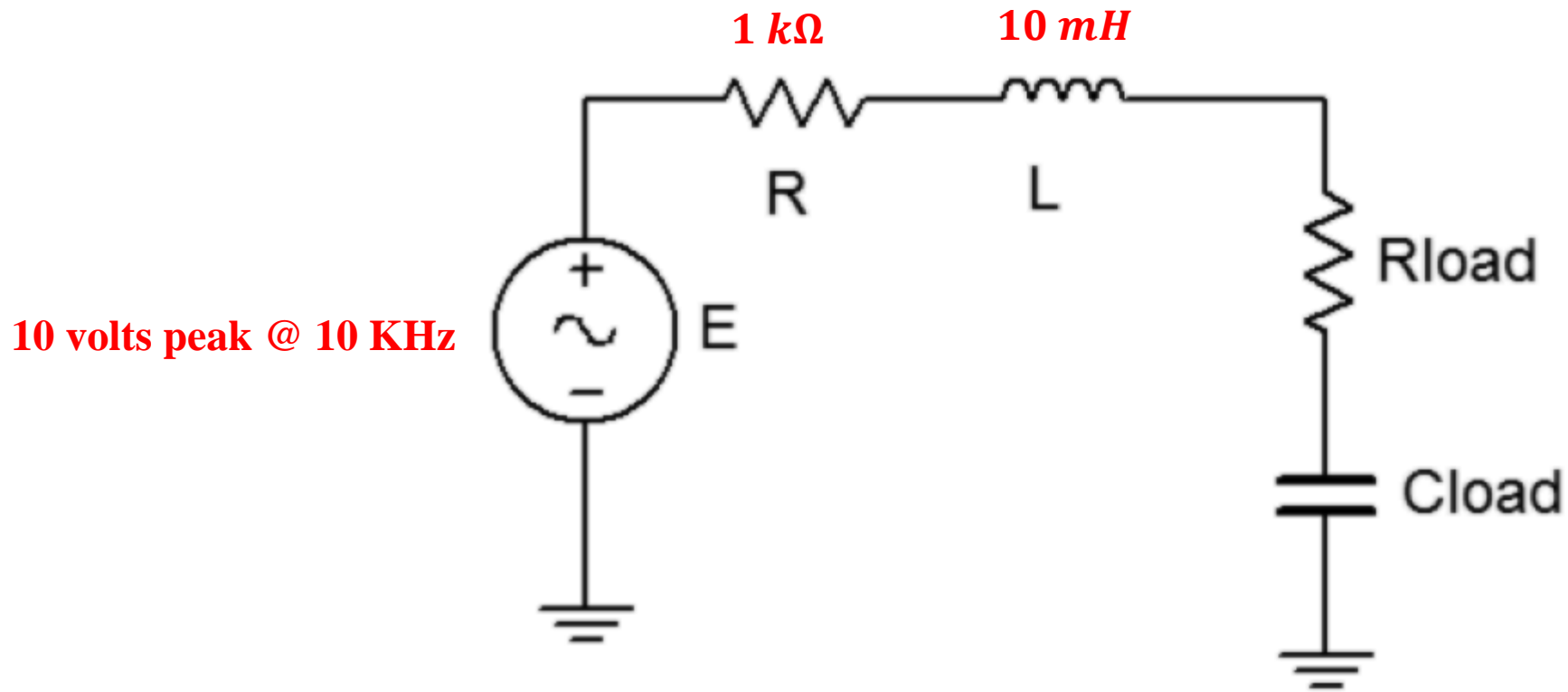


Figure 1

# Procedure: Step 1

- For the circuit shown in Fig. 1, calculate the following:
  - a) The value of the load impedance that will guarantee maximum power transfer
  - b) The value of the resistor needed to realize that circuit
  - c) The value of the capacitor needed to realize that circuit
- Record your answers in table 1

# Procedure: Step 1 – cont.

**Table 1**

Quantity	Value
$Z_{Th}$	
$Z_{load}$ for max power transfer	
$R_{load}$ for max power transfer	
$C_{load}$ for max power transfer	

# Procedure: Step 2

- Use the value of  $C_{load}$  you calculated in Table 1 to fill Table 2 using the resistors values provided in the table

Note 1:  $V_{load_{Theory}} = V_{Th} \times \frac{R_L}{R_L + R_{Th}}$

Note 2:  $V_{load_{Experimental}}$  is the voltage across  $R_L$

Note 3:  $P_{load_{Theory}} = \frac{(V_{load_{Theory}})_{rms}^2}{R_L}$

Note 4:  $P_{load_{Experimental}} = \frac{(V_{load_{Experimental}})^2}{R_L}$



# Procedure: Step 2 – cont.

**Table 2**

$R_{load} (\Omega)$	$V_{load}$ Theory	$V_{load}$ Experimental	$P_{load}$ Theory	$P_{load}$ Experimental
100				
600				
1000				
3000				
10,000				

# Procedure: Step 3

- Use the value of  $R_L$  you calculated in Table 1 to fill Table 3 using the capacitors values provided in the table

Note 1:  $V_{load_{Theory}} = V_{Th} \times \frac{R_L}{R_L + R_{Th}}$

Note 2:  $V_{load_{Experimental}}$  is the voltage across  $R_L$

Note 3:  $P_{load_{Theory}} = \frac{(V_{load_{Theory}})_{rms}^2}{R_L}$

Note 4:  $P_{load_{Experimental}} = \frac{(V_{load_{Experimental}})^2}{R_L}$

# Procedure: Step 3 – cont.

**Table 3**

$C_{load}$	$V_{load}$ Theory	$V_{load}$ Experimental	$P_{load}$ Theory	$P_{load}$ Experimental
10 nF				
47 nF				
0.1 $\mu F$				
0.247 $\mu F$				
0.4 $\mu F$				

## Procedure: Step 4

- Generate a plot of  $P_{load}$  (experimental and theoretical) with respect to  $R_{load}$  and another one for  $P_{load}$  (experimental and theoretical) with respect to  $C_{load}$
- Comment on your plot

# Questions

Q1) In general, given a certain source impedance, what load impedance will achieve maximum load power?

Q2) If the experiment was repeated using a frequency of 5 kHz, how would the graphs change, if at all?