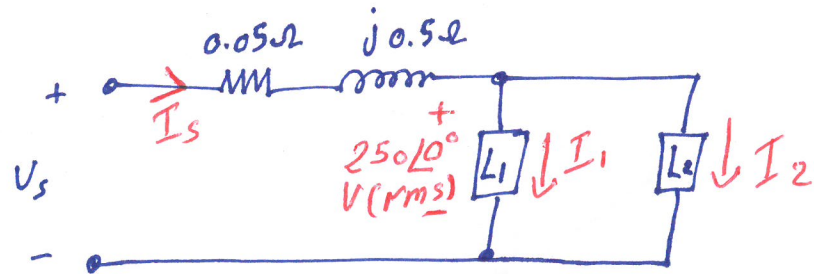


Example 10.6 3

1

* We have the following circuit:



→ Load 1 (L_1) absorbs an average power (P) of 8 kW @ a leading power factor of 0.8

- Leading power factor means that θ is negative.

→ Load 2 (L_2) absorbs 20 kVA @ a lagging power factor of 0.6.

- lagging power factor means that θ is positive.
- From the unit of the absorbed power (VA), we can tell that this is "S", the complex power.

* Solution:

a) We need to determine the power factor of the two loads in parallel.

→ Let us start with the information we have:

$$S = S_1 + S_2$$

a) cont.:

(2)

$$S_1 = P_1 + jQ_1, P_1 = 8000 \text{ W}, \cos(\theta) = 0.8$$

$$S_2 = P_2 + jQ_2, S_2 = 20,000 \text{ VA}, \cos(\theta) = 0.6$$

$$\Rightarrow P_1 = |S_1| \cos(\theta) \Rightarrow 8000 = |S_1| \cos(\theta) = |S_1|(0.8)$$

$$\Rightarrow |S_1| = \frac{8000}{0.8} = 10,000 \text{ VA}$$

$$\Rightarrow Q_1 = |S_1| \sin(\theta)$$

$$\left\{ \begin{array}{l} \cos(\theta) = 0.8 \Rightarrow \theta = 36.87^\circ \\ \sin(36.87^\circ) = 0.6 \end{array} \right.$$

$$Q_1 = 10,000 * (0.6) = 6,000 \text{ VAR}$$

\Rightarrow However, since L_1 has a leading power factor, then "Q" is -ve $\Rightarrow Q_1 = -6,000 \text{ VAR}$.

$$\Rightarrow P_2 = |S_2| \cos(\theta) = 20,000 * (0.6) = 12,000 \text{ W}$$


$$Q_2 = |S_2| \sin(\theta) = 20,000 * (0.8) = 16,000 \text{ VAR}$$

\Rightarrow since L_2 has a Lagging power factor, the "Q" is +ve $\Rightarrow Q_2 = 16,000 \text{ VAR}$.

$$\Rightarrow \left. \begin{array}{l} S_1 = 8000 - j6000 \text{ VA} \\ S_2 = 12000 + j16000 \text{ VA} \end{array} \right\} \Rightarrow \boxed{\begin{array}{l} S = S_1 + S_2 \\ = 20000 + j10000 \text{ VA} \end{array}}$$

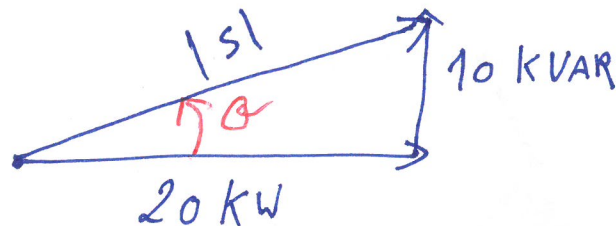a) cont. :

* To find the over all power factor, we can use the power triangle:



$$\theta = \tan^{-1}\left(\frac{10,000}{20,000}\right) = \tan^{-1}(0.5) = 26.565^\circ$$

$$\Rightarrow \text{Thus, power factor} = \cos(26.565) = 0.8944$$

• Since the over all reactive power is positive, $Q = 10,000 \text{ VAR}$, then this is a Lagging power factor.

$$\Rightarrow \boxed{\text{pf} = 0.8944 \text{ lagging.}}$$

b) We need to find the apparent power required to supply the loads, the magnitude of the current I_s , & the average power loss in transmission line.

$$\begin{aligned} * |S| &= |20,000 + j10,000| = \sqrt{(20k)^2 + (10k)^2} \\ &= \boxed{22.36 \text{ kVA.}} \end{aligned}$$

b) Cont.:

(4)

* To find the current I_s , we can use the following equation:

$$S = S_1 + S_2 = (250) I_1^* + (250) I_2^* \\ = 250 (I_1^* + I_2^*)$$

This summation is I_s^*

$$\Rightarrow I_s^* = \frac{S}{250 \angle 0^\circ} = \frac{20,000 + j 10,000}{250 \angle 0^\circ}$$

$$\Rightarrow I_s^* = 80 + j 40 \text{ A}$$

$$\Rightarrow \boxed{I_s = 80 - j 40 \text{ A}}$$

* To find average power loss in the transmission line:

$$P = |I_s|^2 R$$

↳ We use "R" only because we want the average power (real power)


$$|I_s| = |80 - j 40| = \sqrt{80^2 + 40^2} = 89.44 \text{ A}$$

$$\Rightarrow \boxed{P = (89.44)^2 (0.05) = 400 \text{ W.}}$$

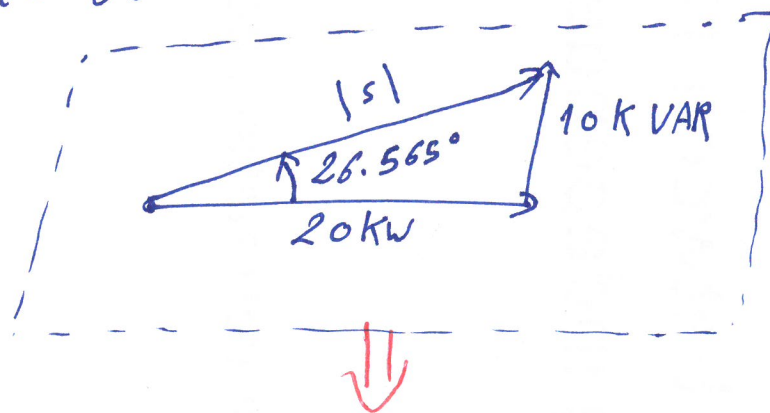c) We are asked to find the value of a capacitor that if added in parallel to the loads L_1 & L_2 , will correct the power factor to "1".


$$PF = 1 = \cos(\theta) \Rightarrow \theta = 0^\circ$$

\Rightarrow Thus, we want the angle θ in the power triangle to be 0° .



\leftarrow This is the original power triangle before adding the capacitor.

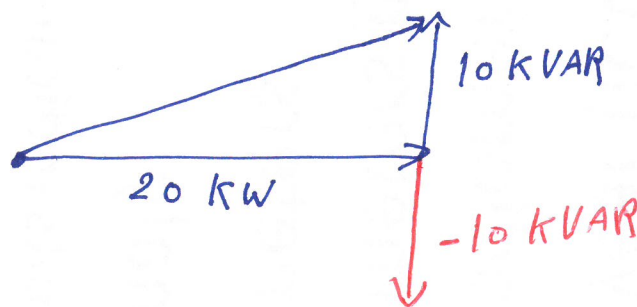* To change " θ " from 26.565° to " 0 ", then the capacitor must provide -10 kVAR



\Rightarrow This will make $\theta = 0^\circ$.

\Rightarrow Thus, Q for the capacitor $= -10 \text{ kVAR}$.

$$Q = \frac{|V_{eff}|^2}{X} \Rightarrow X = \frac{|V_{eff}|^2}{Q} = \frac{(250)^2}{-10 \text{ K}} = -6.25 \Omega$$

Reactance

C) Cont. :

6

⊛ We are given that the frequency = 60 Hz

$$\Rightarrow \omega = 2\pi f = 2\pi(60) = 376.99 \text{ rad/sec.}$$

$$X = \frac{-1}{\omega C} \Rightarrow C = \frac{-1}{\omega X} = \frac{-1}{(376.99)(-6.25)}$$

$$\Rightarrow C = 424.4 \text{ } \mu\text{F}$$

$$= 424.2 \times 10^{-6} \text{ F}$$