

## **EEL 3112c – Circuits 2**

### **Quiz on Chapter 8**


#### **Notes:**

- Write your name on all pages
- Time limit is 20 minutes
- The quiz is closed book and closed notes
- You are allowed to use a calculator
- Show your work not just the final answer
- Your answers must be organized and easy to follow
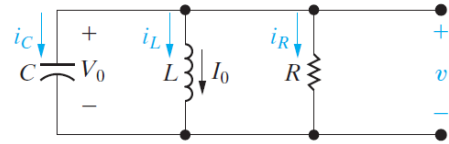
### Problem 1: (5 points)

Suppose the inductor in the circuit shown below has a value of  $10\text{ mH}$ . The voltage response for  $t \geq 0$  is  $v(t) = 40e^{-1000t} - 90e^{-4000t}$  Volts.

- Determine the numerical value for  $\omega_0$ ,  $\alpha$ ,  $C$ , and  $R$  (2 points)
- Find the expression for  $i_R(t)$  (2 points)
- Determine whether this circuit is over, under, or critically damped (1 point)



Hint:  $\alpha = \frac{1}{2RC}$ ,  $\omega_0^2 = \frac{1}{LC}$

### Solution:

$$[a] -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1000$$

$$-\alpha - \sqrt{\alpha^2 - \omega_0^2} = -4000$$

$$\text{Adding the above equations,} \quad -2\alpha = -5000$$

$$\alpha = 2500 \text{ rad/s}$$

$$-2500 \pm \sqrt{2500^2 - \omega_0^2} = -1000 \quad \text{so} \quad \sqrt{2500^2 - \omega_0^2} = 1500$$

$$\therefore -\omega_0^2 = 1500^2 - 2500^2 \quad \text{thus} \quad \omega_0 = 2000 \text{ Rad/sec}$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(0.01)C} = 2000^2 \quad \text{so} \quad C = \frac{1}{(0.01)2000^2} = 25 \mu\text{F}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2R(25 \times 10^{-6})} = 2500 \quad \text{so} \quad R = \frac{1}{2(25 \times 10^{-6})(2500)} = 8 \Omega$$

$$[b] i_R = \frac{v(t)}{R} = 5e^{-1000t} - 11.25e^{-4000t} \text{ A}, \quad t \geq 0^+$$

C)

The Circuit is	When	Qualitative Nature of the Response
Overdamped	$\alpha^2 > \omega_0^2$	The voltage or current approaches its final value without oscillation
Underdamped	$\alpha^2 < \omega_0^2$	The voltage or current oscillates about its final value
Critically damped	$\alpha^2 = \omega_0^2$	The voltage or current is on the verge of oscillating about its final value