

Computer Simulation

15. Build the circuit of Figure 8.1 in a simulator. Using Transient Analysis, determine the voltage across the inductor and compare the magnitude and phase to the theoretical and measured values recorded in Table 8.2.

Data Tables

Circuit 1

Ω	Theory	Experimental	% Deviation
X_C	-1665.7		
X_L	628.00		
$R X_L$	$285.06 + j445.7$	$302.93 + j404.5$	8.48
Z_T Magnitude	1252.9	1282.67	2.38
$Z_T \theta$	-76.85	-75.528	1.72

Table 8.1

$$\begin{array}{l} 128.7^\circ \\ -14.47^\circ \end{array}$$

	Theory Mag	Theory θ°	Exp Mag	Exp Delay	Exp θ	% Dev Mag	% Dev θ
V_{LR}	2.111 V	134.2	1.970 V	-35.75 ms	-93.1°	6.64	4.13
V_C	6.647 V	-13.15	6.493 V	-95.98 ms	-13.56°	2.32	10.04
i_{in}	3.992 mA	76.85°	3.898 mA	N/A	75.528	2.32	1.72

Nominal: Measured: Table 8.2

$10 \text{ nF} \rightarrow 9.555 \text{ nF}$ V_{LR} Simulator
mag. 2.1418 V

10 mH delay 63.2 ms

$1 \text{ k}\Omega$ phase θ 137.49°

~~610~~ Ω 10.074Ω

$K 10 \Omega$ 10.072Ω

Phasor plots sep. page

Circuit 2

Ω	Theory	Experimental	% Deviation
X_C	-1665.67		
X_L	628.00		
$R + X_L$	981.83 + j628	1207 + j660.5	21.12%
Z_T Magnitude	2090.93	1454.5	30.44
$Z_T \theta$	75.1767	77.472	3.07

Table 8.3

mA	Theory Mag	Theory θ	Exp Mag	Exp Delay	Exp θ	% Dev Mag	% Dev θ
i_{LR}	4.290mA	-32.604°	3.878mA	-92.44ms	32.97°	9.60	5.48
i_C	3.001mA	90°	2.8017mA	-24.46ms	-80.82°	6.40	2.26
i_{in}	2.391mA	-75.17°	3.4376mA	-3.48ms	713.38°	43.76	3.07

Table 8.4

-30.816
88.056
-77.472

Questions

1. Is the phase relationship between circuit voltages or currents in a series-parallel AC circuit necessarily a right-angle relationship?

No, due to mixed positions of the 3 components.

2. Based on measurements, do KVL and KCL apply to the tested circuits (show work)?

see separate page 56

$$2. \quad 1.070 \angle 128.7^\circ + 6.493 \angle -14.472^\circ = 5 \angle 0^\circ \text{ V}$$

$$-1.232 +; 2.537 + 6.287 \angle; 1.623 \approx 5 \text{ V} \quad \text{circuit 2}$$

Circuit 2:

$$0.003878 \angle -30.816^\circ + 0.0028097 \angle 88.056^\circ = 0.0034376 \angle -77.472 \text{ A}$$

$$0.00333 -; 0.00799 + 9.9 \times 10^{-5} \text{ A} +; 0.002808 \approx 0.000746 -; 0.00336 \text{ A}$$


3. In general, how would the phasor diagram of Figure 8.1 change if the frequency was raised?

The phasors ~~diagram~~ would rotate until the input current vector with frequency increase is parallel to the imaginary axis.

4. In general, how would the phasor diagram of Figure 8.2 change if the frequency was lowered?


The phasors would rotate until the input current vector with decreasing frequency matches the real axis in parallel.

Phasor Plots

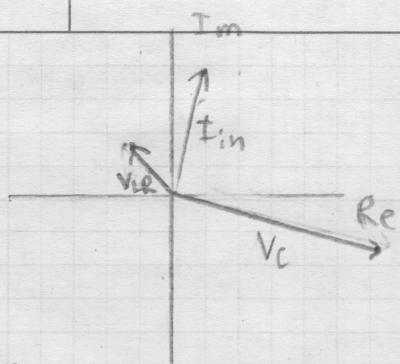


$$1 \text{ div} = 1 \text{ V} \\ = 2 \text{ mA}$$

$C + R \parallel L$


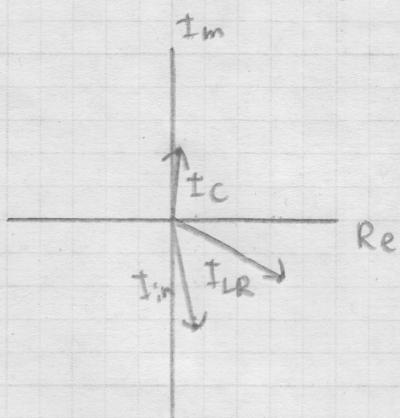


$C \parallel R + L$

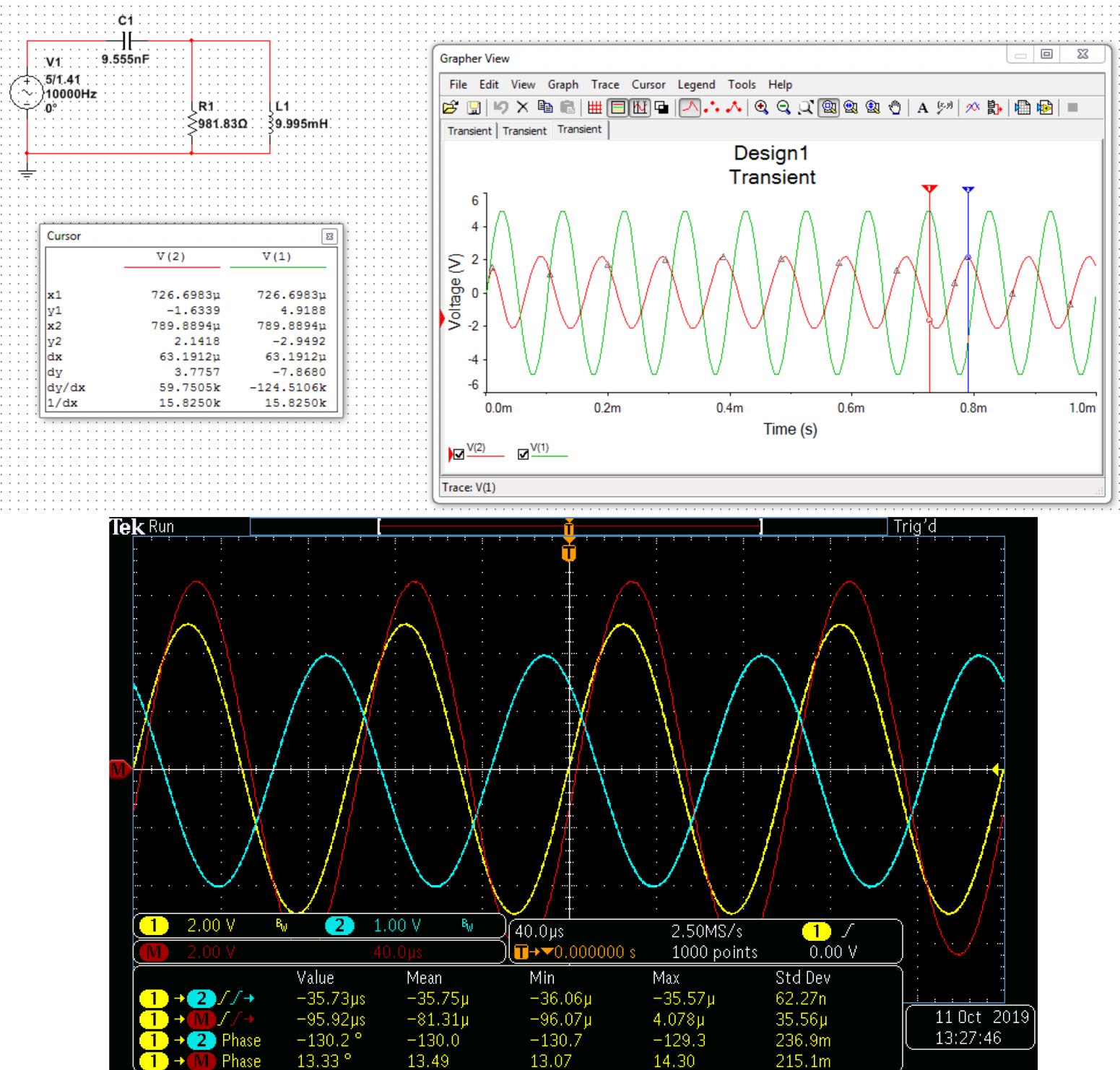Peter A. Dranishnikov Lab 7 (#8 Manual ref.) EEL3112C s01



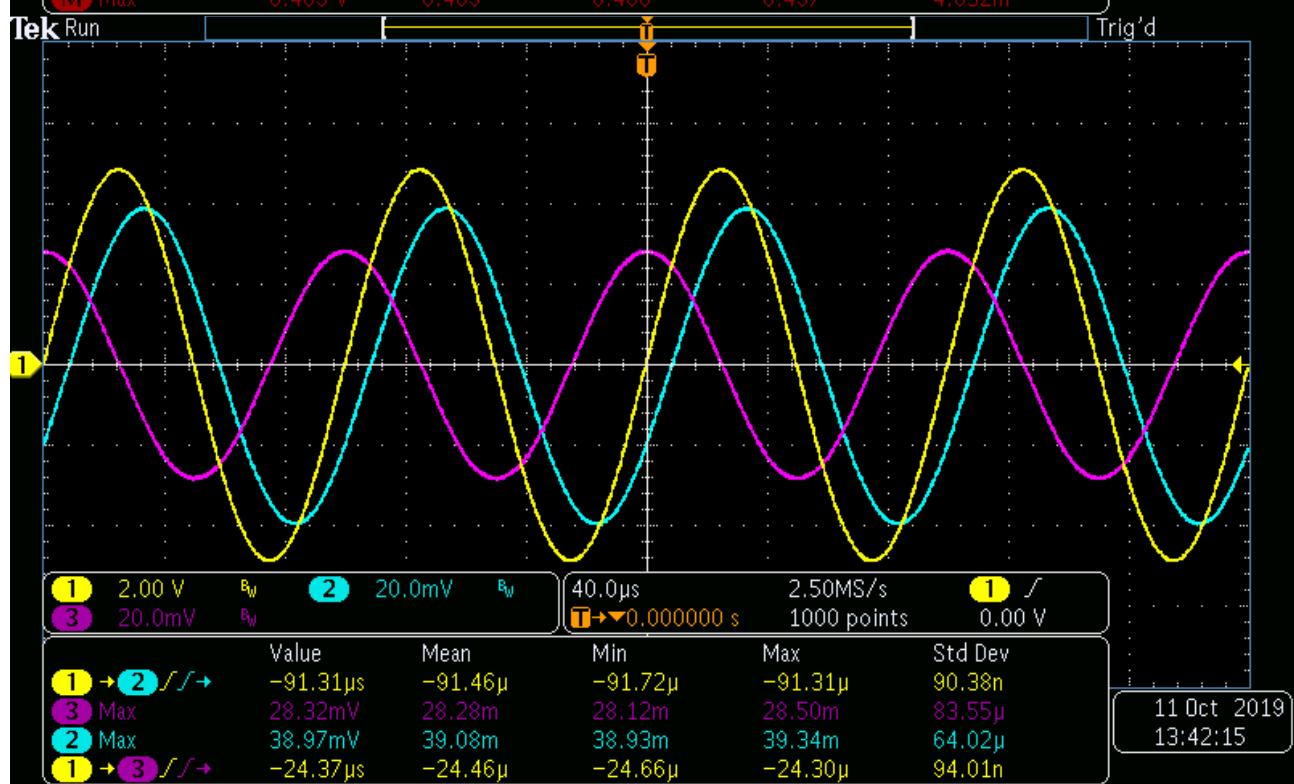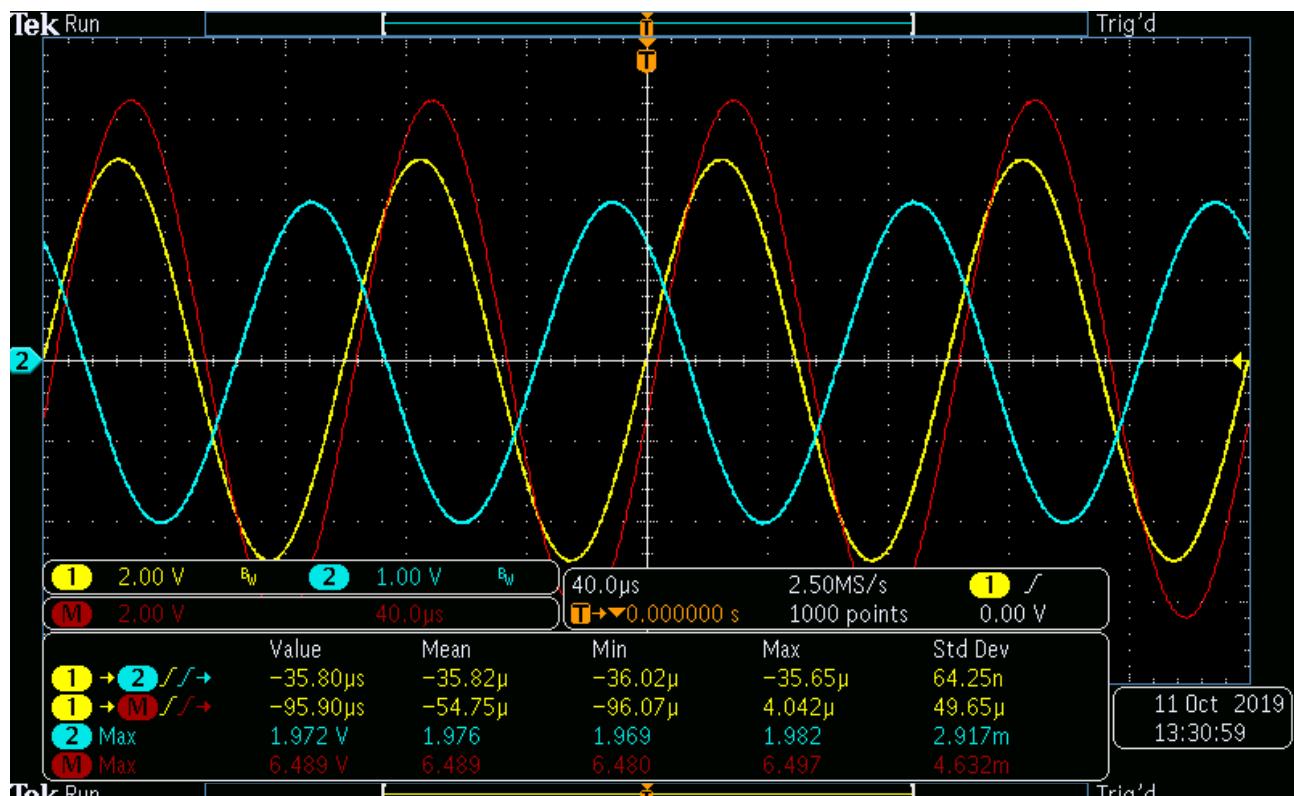Peter A. Dranishnikov Lab 7 (#8 Manual ref.) EEL3112C s01



Peter A. Dranishnikov Lab 7 (#8 Manual ref.) EEL3112C s01

